
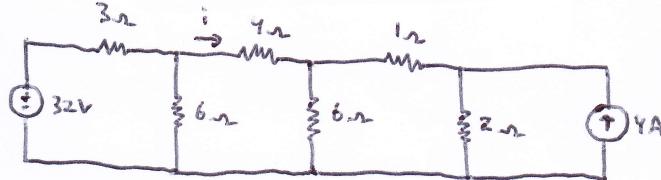



1). Find i using source transformation

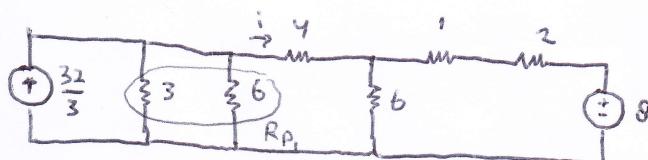



Answer:



$$R_{P_1} = \frac{3 \times 6}{3+6} = 2$$

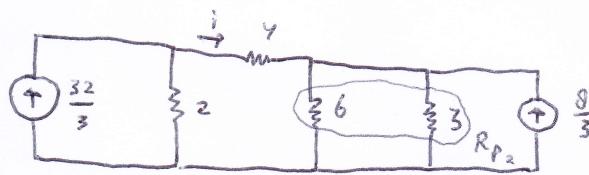


$$R_{P_2} = \frac{6 \times 3}{6+3} = 2$$

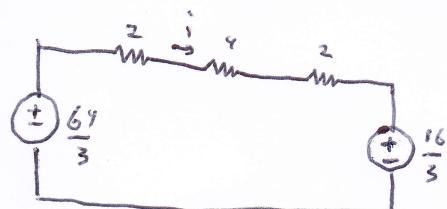
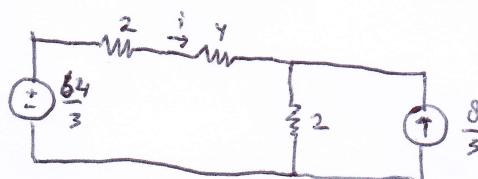


$$i = \frac{16}{8} = 2A$$

2). Find i using source transformation

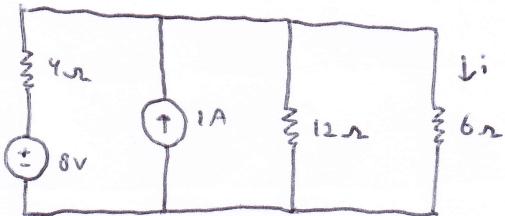


Answer:

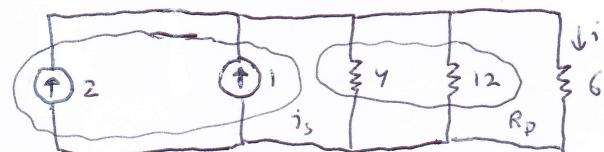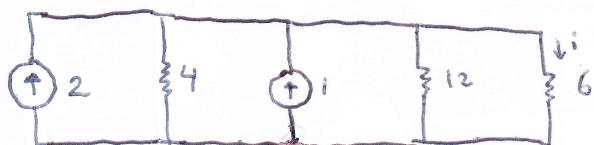


$$i_S = 3$$
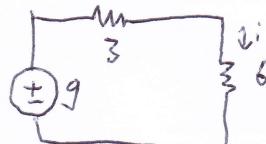
$$R_P = \frac{4 \cdot 12}{4+12} = \frac{4 \cdot 12}{16} = 3$$




$$i = \frac{9}{3+6} = 1A$$




3). Find v using source transformation

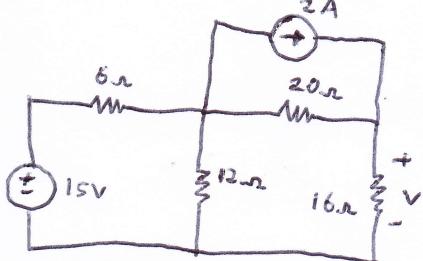

Answer

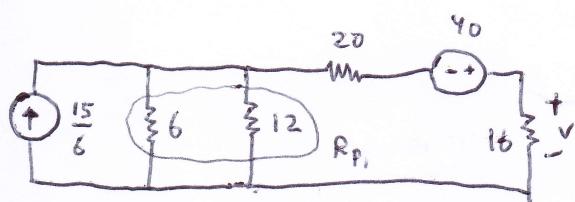

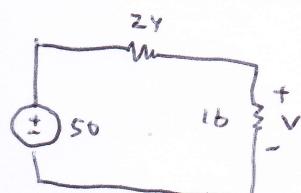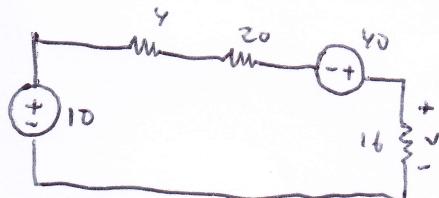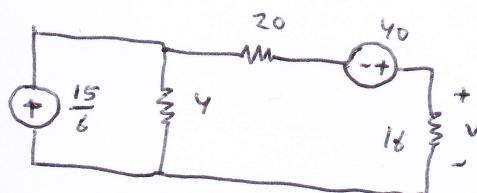
$$R_{P_i} = \frac{6 \cdot 12}{6 + 12} = \frac{1}{2} \cdot 12 = 6 \Omega$$







$$V = 50 \times \frac{16}{2Y + 16} = 50 \times \frac{16}{2 \cdot 4} = 20 \text{ Volts}$$

4). Find v using source transformation

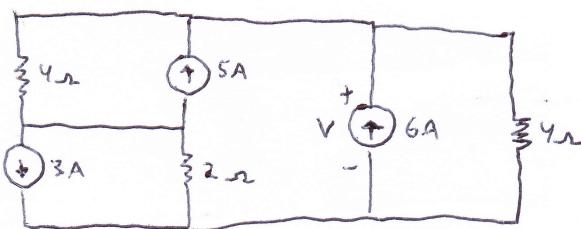


Answer

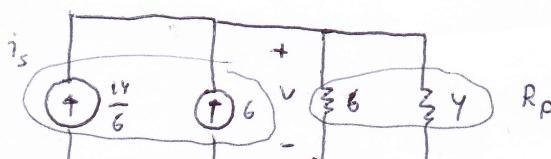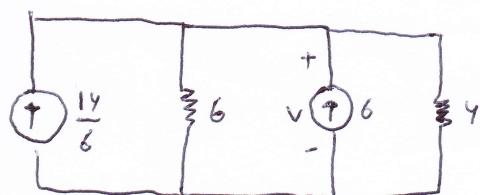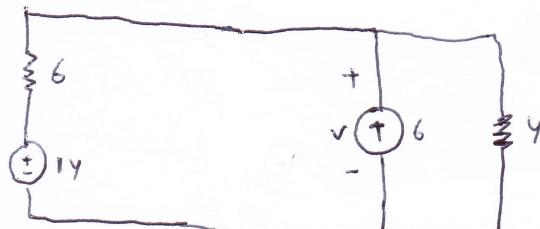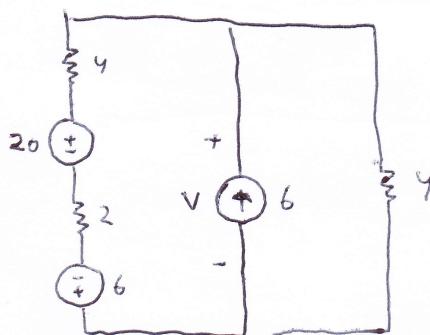


$$i_s = \frac{14}{6} + \frac{36}{6} = \frac{50}{6}$$
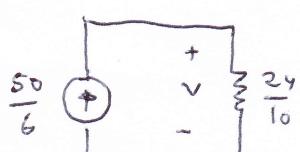
$$R_p = \frac{6 \times 4}{10} = \frac{24}{10}$$







$$V = \frac{50}{6} \times \frac{24}{10} = \underline{\underline{20 \text{ Volts}}}$$

5). Find i using source transformation

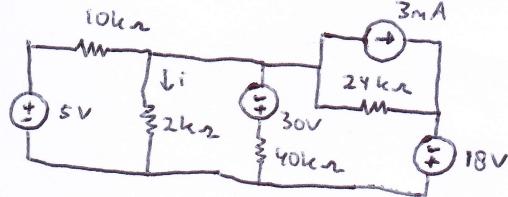

Answer:

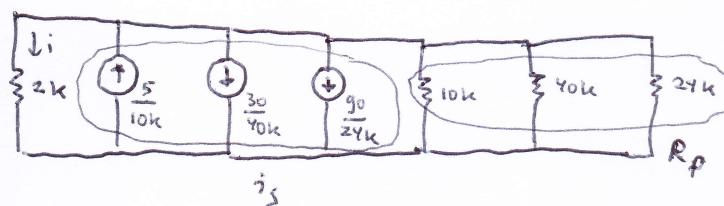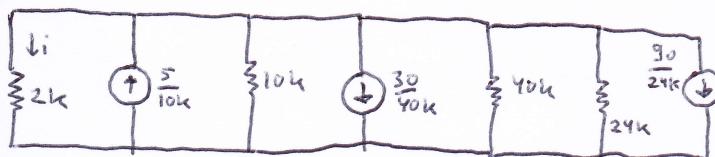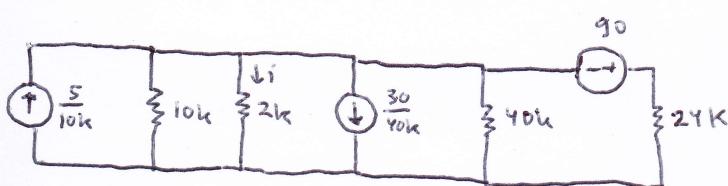
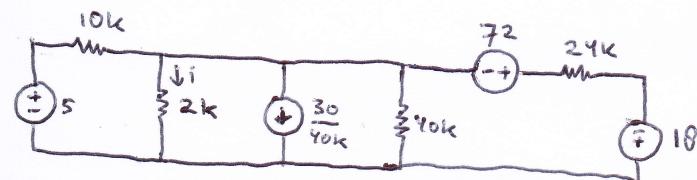


$$i_s = \frac{5}{10k} - \frac{30}{40k} - \frac{90}{24k} = \frac{60}{120k} - \frac{90}{120k} - \frac{450}{120k} = -\frac{480}{120k}$$

$$= -4mA$$

$$\frac{1}{R_p} = \frac{1}{10k} + \frac{1}{40k} + \frac{1}{24k} = \frac{12+3+5}{120k} = \frac{20}{120k}$$

$$R_p = 6k$$

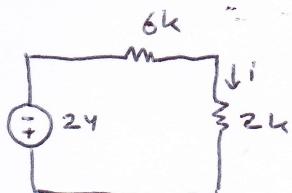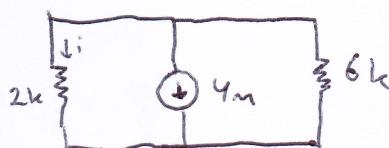

$$i = \frac{24}{8k} = 3mA$$