
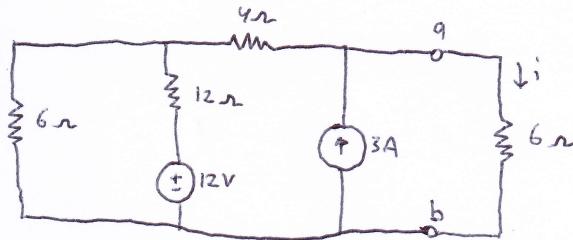


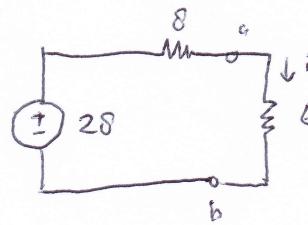1). Replace the network to the left of terminals a-b by its Thevenin equivalent and use the result to find i.




Thevenin Circuit





$$i = \frac{28}{8+6} = \frac{28}{14} = 2A$$

Answer:

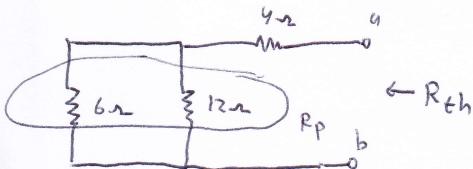
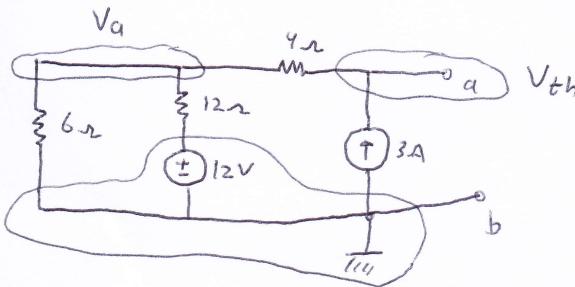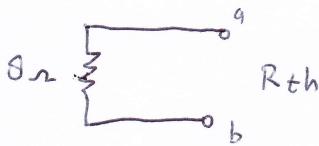
$$R_p = \frac{6 \times 12}{6+12} = \frac{6 \times 12}{18} = 4$$



Node  $V_a$ :

$$\frac{V_a}{6} + \frac{V_a - 12}{12} + \frac{V_a - V_{th}}{4} = 0 \quad \times 12$$

$$2V_a + V_a - 12 + 3V_a - 3V_{th} = 0$$

$$6V_a = 12 + 3V_{th}$$

$$V_a = 2 + \frac{1}{2}V_{th} \dots (1)$$

Node  $V_{th}$ :

$$\frac{V_{th} - V_a}{4} - 3 = 0$$

$$V_{th} - V_a = 12 \dots (2)$$


(1) & (2):

$$V_{th} - (2 + \frac{1}{2}V_{th}) = 12$$


$$\frac{1}{2}V_{th} = 14$$

$$V_{th} = 28$$

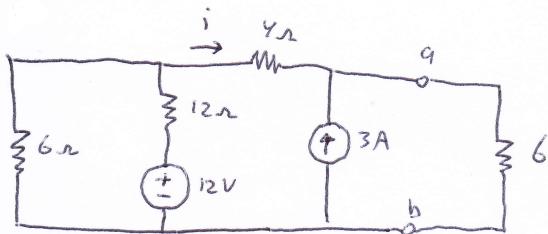
2). Find the Thevenin equivalent of everything except the  $4\text{-}\Omega$  resistor and use the result to find  $i$



Answer

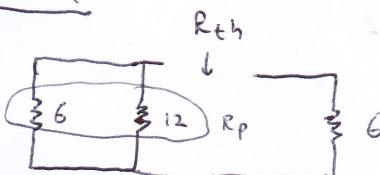
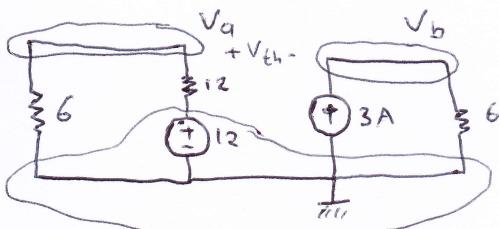
$$R_p = \frac{6 \times 12}{6 + 12} = \frac{6 \times 12}{18} = 4$$



node  $V_a$ :

$$\frac{V_a}{6} + \frac{V_a - 12}{12} = 0 \times 12$$

$$2V_a + V_a = 12$$

$$V_a = 4 \text{ volt}$$


node  $V_b$ :

$$-3 + \frac{V_b}{6} = 0$$


$$V_b = 18 \text{ volt}$$

$$V_{th} = V_a - V_b = -14 \text{ volt}$$


Thevenin circuit:

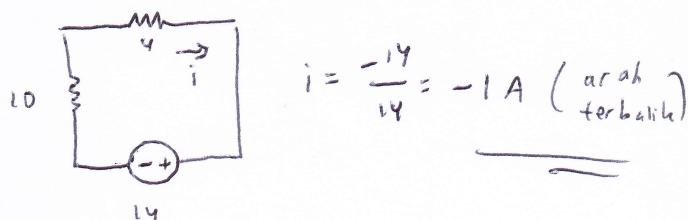

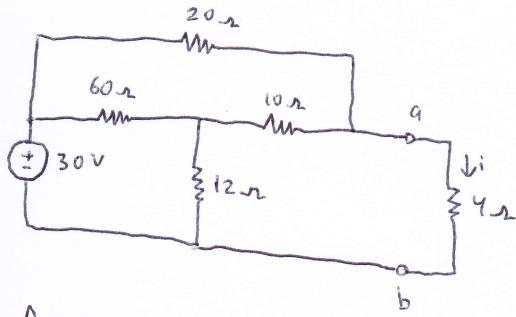
3. Find the Norton equivalent of the circuit to the left of terminal a-b, and use the result to find  $i$ .




Answer

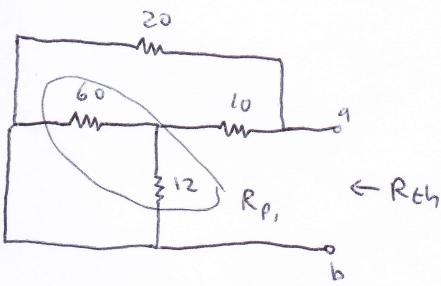

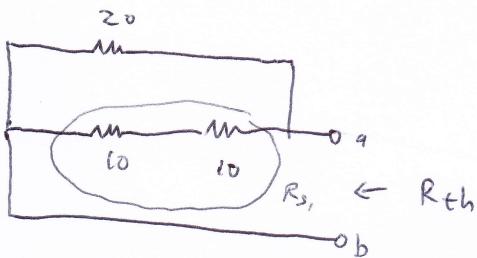
$$R_{th} = \frac{60 \times 12}{60 + 12} = \frac{60 \times 12}{72} = 10 \Omega$$



$$R_{th} = 20 \Omega$$

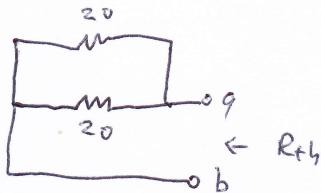
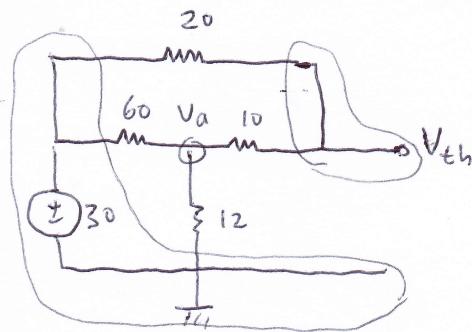
$$R_{th} = \frac{20 \times 20}{20 + 20} = 10 \Omega$$



Node  $V_a$ :

$$\frac{V_a - 30}{60} + \frac{V_a}{12} + \frac{V_a - V_{th}}{10} = 0 \quad \times 60$$

$$V_a - 30 + 5V_a + 6V_a - 6V_{th} = 0$$

$$12V_a - 6V_{th} = 30$$

$$2V_a - V_{th} = 5 \quad \dots (1)$$

Node  $V_{th}$ :

$$\frac{V_{th} - V_a}{10} + \frac{V_{th} - 30}{20} = 0 \quad \times 20$$

$$2V_{th} - 2V_a + V_{th} - 30 = 0$$


$$-2V_a + 3V_{th} = 30 \quad \dots (2)$$

(1) & (2):

$$\begin{aligned} 2V_a - V_{th} &= 5 \\ -2V_a + 3V_{th} &= 30 \end{aligned} \quad \begin{aligned} \hline & \\ & \end{aligned} \quad \begin{aligned} 2V_{th} &= 35 \\ V_{th} &= 17.5 \end{aligned}$$


$$i_N = \frac{V_{th}}{R_{th}} = \frac{17.5}{10} = 1.75 \text{ A}$$

Norton circuit:

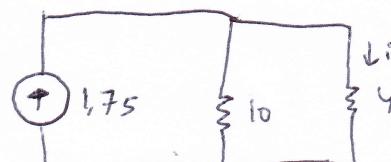


$$i = \frac{10}{10 + 4} \cdot 1.75 = 1.25 \text{ A}$$

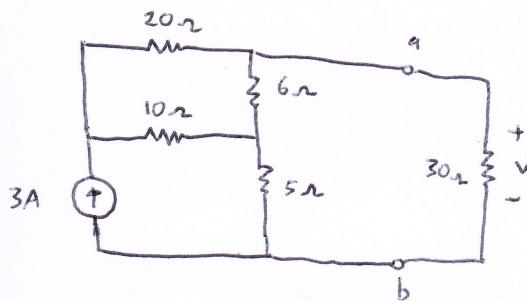
4). Find the Norton equivalent of the circuit to the left of terminal a-b, and use the result to find v



Answer

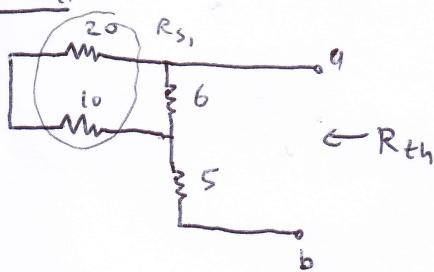


$$R_{S_1} = 30$$

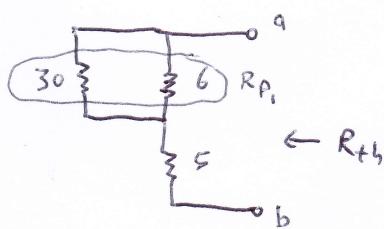

$$R_{P_1} = \frac{6 \times 30}{6 + 30} = \frac{6 \times 30}{36} = 5\Omega$$

$$R_{th} = 10\Omega$$

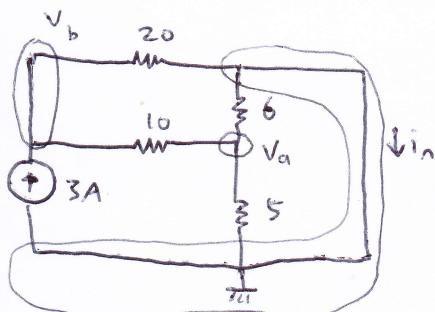

node V<sub>a</sub>:

$$\frac{V_a}{5} + \frac{V_a - V_b}{10} + \frac{V_a}{6} = 0 \quad \times 60$$

$$12V_a + 6V_a - 6V_b + 10V_a = 0$$

$$28V_a - 6V_b = 0$$

$$14V_a - 3V_b = 0 \quad \dots (1)$$

node V<sub>b</sub>:

$$\frac{V_b}{20} + \frac{V_b - V_a}{10} - 3 = 0 \quad \times 20$$

$$V_b + 2V_b - 2V_a - 60 = 0$$

$$-2V_a + 3V_b = 60 \quad \dots (2)$$

(1) & (2):

$$14V_a - 3V_b = 0$$

$$-2V_a + 3V_b = 60 \quad +$$

$$12V_a = 60$$

$$V_a = 5 \text{ volt}$$


Dari (2):

$$3V_b = 60 + 2V_a$$

$$V_b = \frac{60 + 2 \cdot 5}{3} = \frac{70}{3}$$

$$i_n = \frac{V_a}{6} + \frac{V_b}{20} = \frac{5}{6} + \frac{70}{3 \cdot 20} = \frac{12}{6} = 2A$$


Norton circuit:

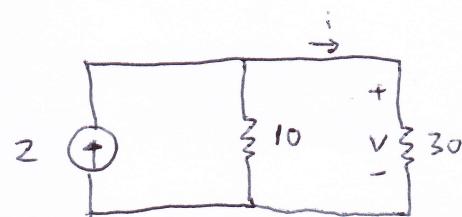


$$i = \frac{10}{10+30} \cdot 2 = \frac{10}{40} \cdot 2 = \frac{1}{2}$$

$$V = 30 \cdot i = 30 \cdot \frac{1}{2} = 15 \text{ volt}$$

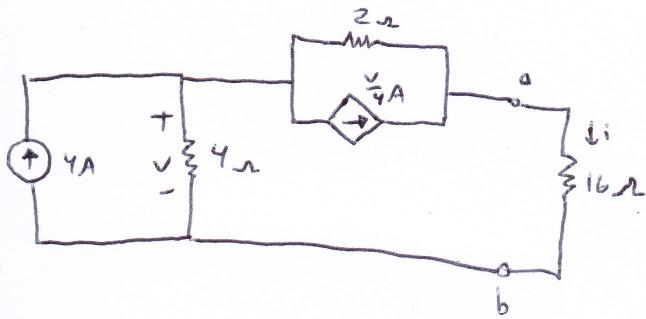5). Find  $i$  by replacing the network to the left of terminals a-b by its Norton equivalent.



Answer

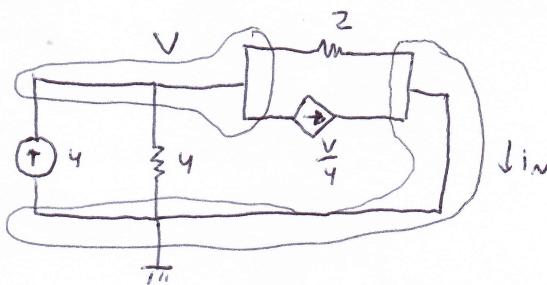

node  $V$ :

$$-4 + \frac{V}{4} + \frac{V}{4} + \frac{V}{2} = 0 \quad \times 4$$

$$V + V + 2V = 16$$


$$4V = 16$$

$$V = 4 \text{ volt}$$

$$i_N = \frac{V}{2} + \frac{V}{4} = 2 + 1 = 3 \text{ A}$$

$$R_{th} = \frac{V_{th}}{i_N} = \frac{24}{3} = 8 \Omega$$

Norton circuit:

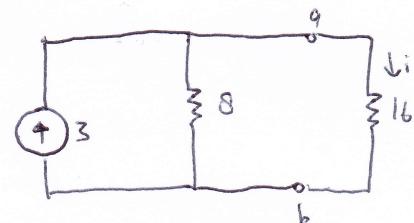

$$i = \frac{8}{8+16} \times 3 = \frac{8}{24} \times 3 = 1 \text{ A}$$

node  $V_{th}$ :

$$-4 + \frac{V}{4} + \frac{V}{4} + \frac{V - V_{th}}{2} = 0 \quad \times 4$$

$$V + V + 2V - 2V_{th} = 16$$

$$4V - 2V_{th} = 16$$

$$2V - V_{th} = 8 \quad \dots (1)$$

node  $V_{th}$ :

$$\frac{V_{th} - V}{2} - \frac{V}{4} = 0 \quad \times 4$$

$$2V_{th} - 2V - V = 0$$

$$-3V + 2V_{th} = 0 \quad \dots (2)$$

(1) & (2):

$$\begin{array}{l} 2V - V_{th} = 8 \\ -3V + 2V_{th} = 0 \end{array} \quad \left| \begin{array}{l} \times 3 \\ \times 2 \end{array} \right.$$

$$6V - 3V_{th} = 24$$


$$-6V + 4V_{th} = 0$$

$$\hline +$$

$$V_{th} = 24$$

Soal 2 Latihan

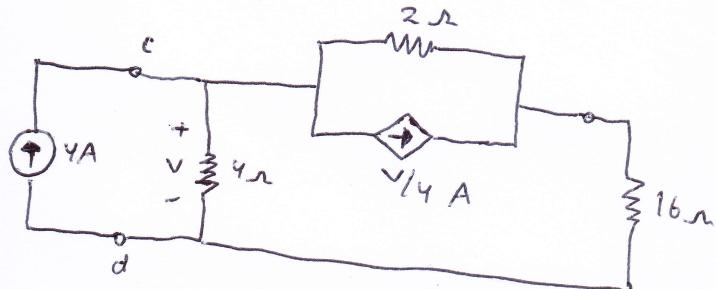
- 1). Replace the network to the right of terminals c-d by its Thevenin equivalent and use the result to find v



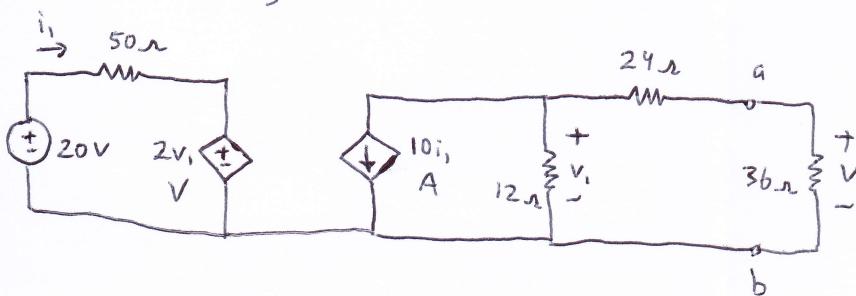- 2). Replace the circuit to the left

of terminals a-b by its

Thevenin equivalent, and use the result to find v



- 3). Replace the circuit to the left

of terminals a-b by its Thevenin

equivalent and use the result

to find v

