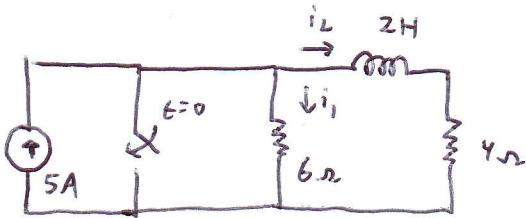


Ralat bagi TE-1


1)



Jika $i_1(0^-) = 2A$ tentukan $i_L(0^-)$, $i_L(0^+)$, $i_1(0^+)$ dan $\frac{di_L(0^+)}{dt}$


Jawab:

Rangk. saat $t=0^-$

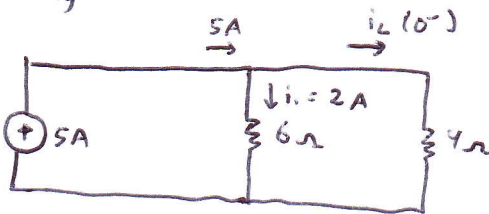

$$i_L(0^-) = 5 - 2 = 3A$$

Rangk. saat $t=0^+$

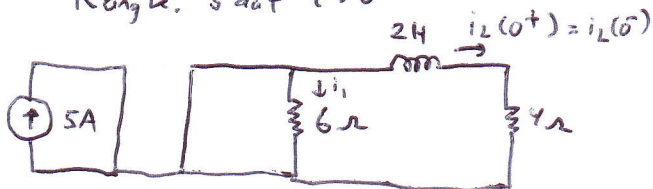

$$i_1(0^+) = 0 \text{ Karena } R=6\Omega \text{ short}$$

Rangkaian diatas dapat digambar

sbb:




Menggunakan KVL:

$$L \frac{di_L}{dt} + 4 \cdot i_L = 0 \quad i_L(0^+) = 3A$$

$$2 \frac{di_L}{dt} + 4 \cdot 3 = 0$$

$$\frac{di_L}{dt} = -\frac{12}{2} = -6 \text{ A/s}$$

2).

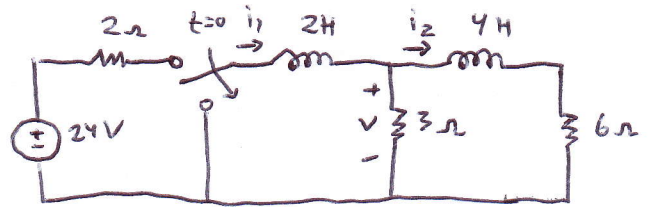


Rangkaian steady state saat $t=0^-$.

Carilah V , i_1 , i_2 , $\frac{di_1}{dt}$ dan $\frac{di_2}{dt}$ saat $t=0^+$

Jawab:

Rangk. saat $t=0^-$

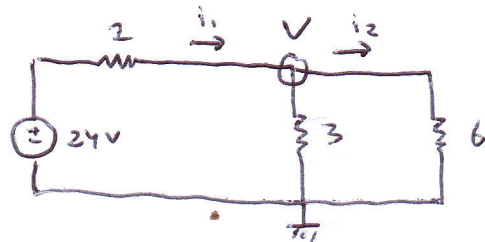

node V:

$$\frac{V-24}{2} + \frac{V}{3} + \frac{V}{6} = 0 \quad \times 6$$


$$3V - 72 + 2V + V = 0$$

$$V = \frac{72}{6} = 12$$

$$i_1 = \frac{24-12}{2} = 6A$$

$$i_2 = \frac{12}{6} = 2A$$

Rangk. saat $t=0^+$

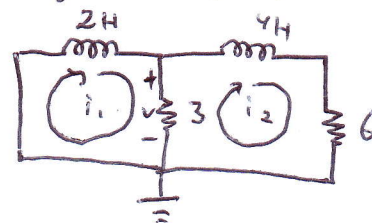

$$i_1(0^+) = i_1(0^-) = 6A$$

$$i_2(0^+) = i_2(0^-) = 2A$$

$$V = 3(i_1 - i_2) = 12V$$

Loop i_1 :

$$2 \frac{di_1}{dt} + V = 0$$

$$\frac{di_1}{dt} = -\frac{12}{2} = -6 \text{ A/s}$$

Loop i_2 :

$$-V + \frac{di_2}{dt} + 12 = 0$$

$$\frac{di_2}{dt} = 0$$