


## Bab 6 : Interfacing dan Pengkondisi Sinyal

Dr. Ir. Yeffry Handoko Putra, M.T

3

### SISTEM PENGUKURAN

signal conditioning

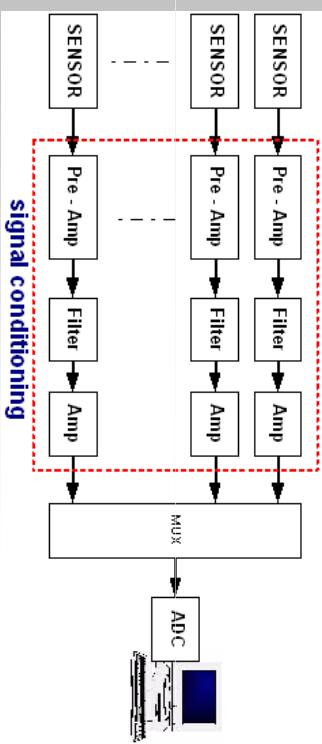


Sistem multisensor dengan display digital

### Sistem Instrumentasi



2

### SISTEM PENGUKURAN

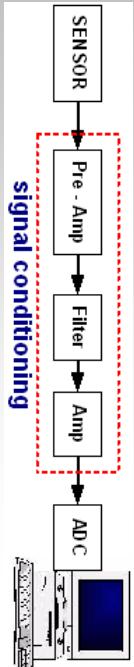


Sistem dengan transmisi data & display digital

4

### SISTEM PENGUKURAN

monitoring system

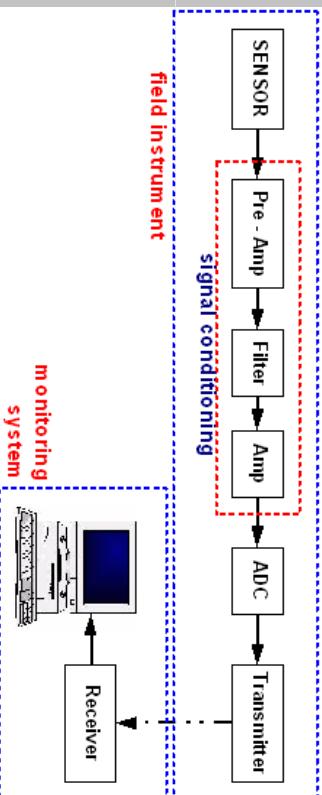

Sistem digital dengan transmisi data


### Sistem Instrumentasi



Sistem Interfacing Instrumentasi  
Sistem dengan display digital


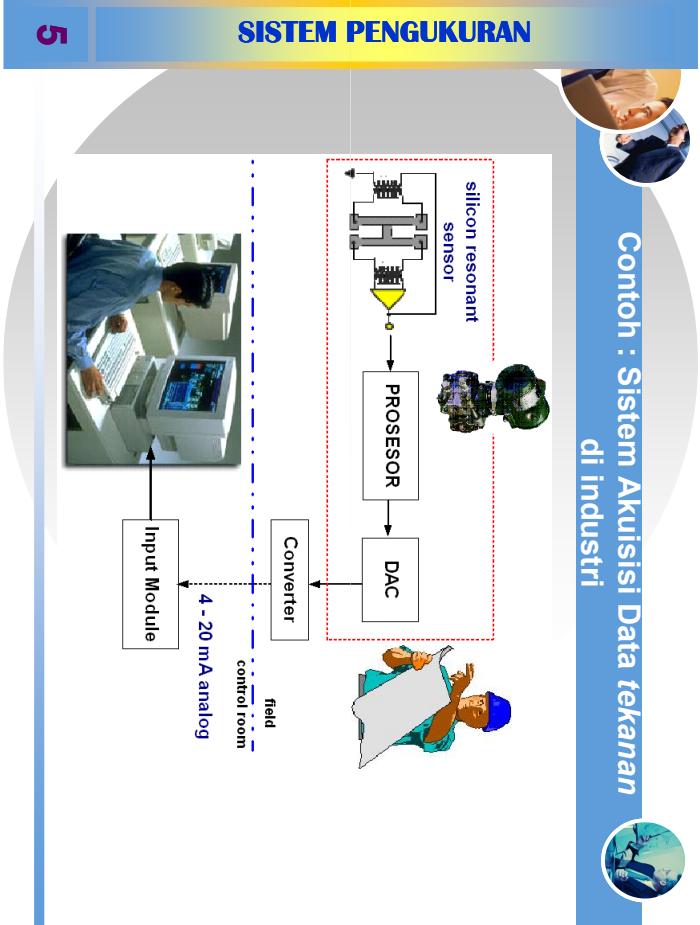
## Contoh : Sistem Akuisisi Data tekanan di industri



7


## SISTEM PENGUKURAN

### Elemen Sistem Instrumentasi dengan Pengkondisi Sinyal

- ❖ **Sensor**
- ❖ **Signal Conditioning (pengkondisi sinyal)**
  - Amplifier
  - Filter
- ❖ **Signal Processing (pemroses sinyal)**
  - Multiplexing
  - Analog – Digital Converter
  - Digital – Analog Converter
- ❖ **Data Presentation (display)**

5


## SISTEM PENGUKURAN

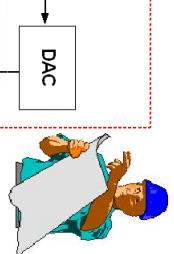

8

## SISTEM PENGUKURAN

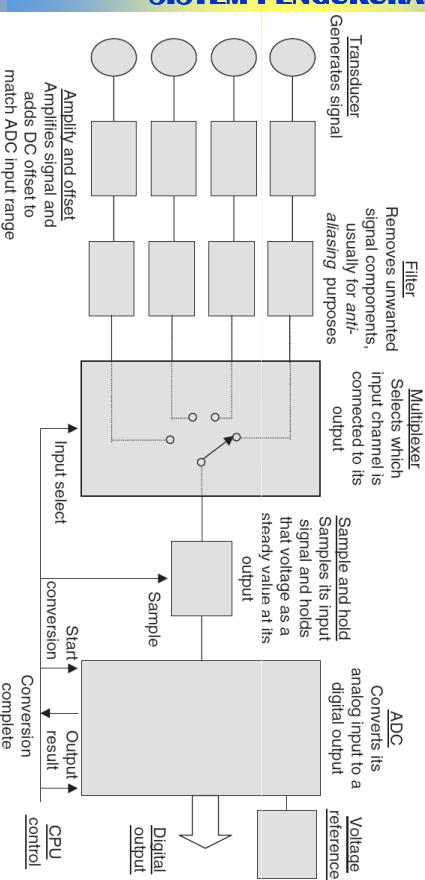
### Elements of a data acquisition system



6

## SISTEM PENGUKURAN

# ELEMEN INSTRUMENTASI

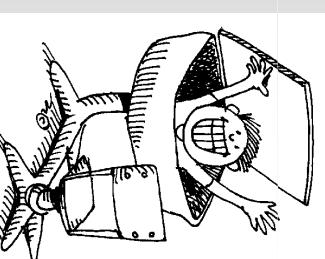





## PENGKONDISI SINYAL - Amplifier

### Amplifier

- Operational Amplifier
- Instrument Amplifier

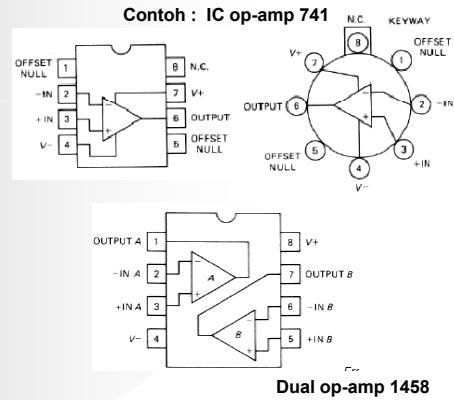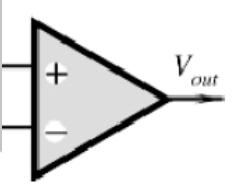
### OPERATIONAL AMPLIFIER

- Primary op-amp terminal
  - ▶ Inverting input
  - ▶ Non-inverting input
  - ▶ Output
  - ▶ Power supply


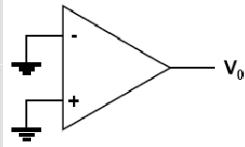
## Amplifier : Op - Amp

- ❖ Zero noise contribution
- ❖ Zero DC output offset
  - *Output offset* merupakan tegangan output pada saat kedua input di-ground (nol)




- Infinite bandwidth
- Differential inputs that stick together



## Amplifier : Op - Amp



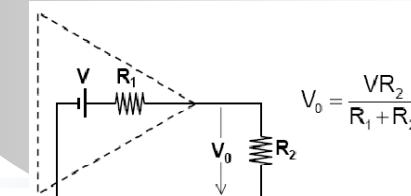
### Karakteristik Op-Amp Ideal

- ❖ Infinite open loop voltage gain
  - *Open loop gain* adalah *gain* op-amp tanpa umpan balik
  - Ideal open loop gain : tidak terhingga
- ❖ Infinite input impedance
  - Arus input adalah NOL
  - Beberapa *low grade op-amp* memiliki arus input dalam orde mA
- ❖ Zero output impedance
  - Beberapa op-amp memiliki *output impedance* sekitar 100 – 200  $\Omega$


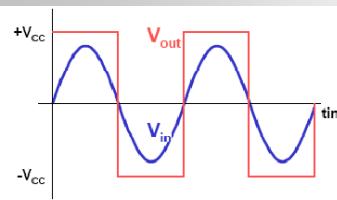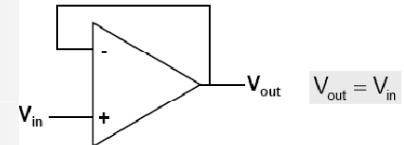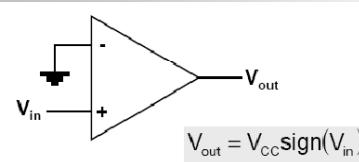
## Amplifier : Rangkaian Op - Amp

- ❖ Voltage comparator
- ❖ Voltage follower




15

## SISTEM PENGUKURAN




### Amplifier : Rangkaian Op - Amp

❖ Integrating amplifier

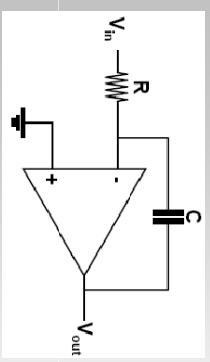

❖ Differentiating amplifier

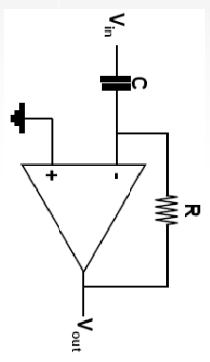

$$V_{out} = -\frac{1}{j\omega CR} V_{in} = -\frac{1}{RC} \int V_{in} dt$$

$$V_{out} = -\frac{R}{j\omega C} V_{in} = -RC \frac{dV_{in}}{dt}$$


13

## SISTEM PENGUKURAN




### Amplifier : Rangkaian Op - Amp

❖ Non-inverting amplifier

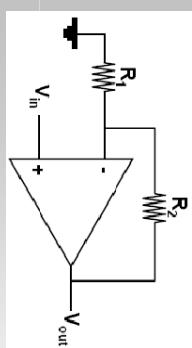

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

❖ Inverting amplifier

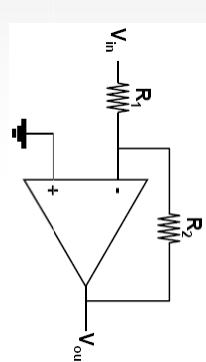

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$


16

## SISTEM PENGUKURAN




### Amplifier : Rangkaian Op - Amp

❖ Current to Voltage converter

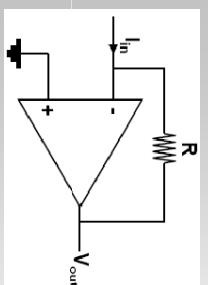

$$V_{out} = -I_{in} R$$

❖ Voltage to Current converter

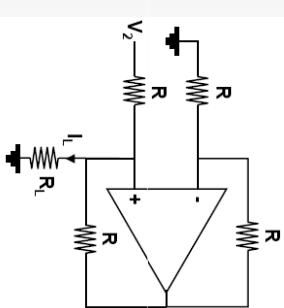

$$I_L = \frac{V_2}{R}$$

14


## SISTEM PENGUKURAN



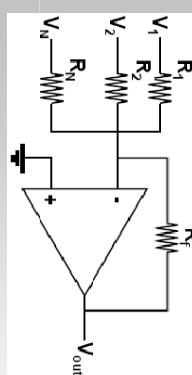
### Amplifier : Rangkaian Op - Amp

❖ Summing amplifier

$$V_{out} = -\left(V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + \dots + V_N \frac{R_f}{R_N}\right)$$



❖ Differential amplifier

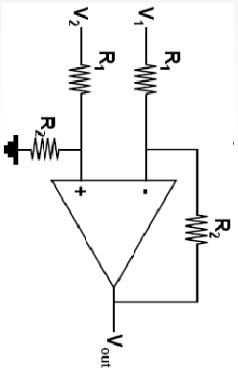


$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$




## Amplifier : Instrumentation Amplifier

- Differential Amplifier

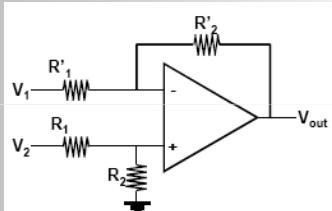


- Tegangan COMMON MODE & DIFFERENCE MODE

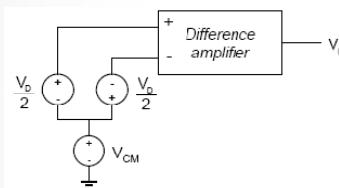


$$V_{CM} = \frac{V_2 + V_1}{2}$$

$$V_D = V_2 - V_1$$

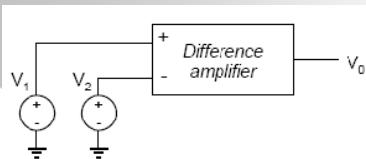
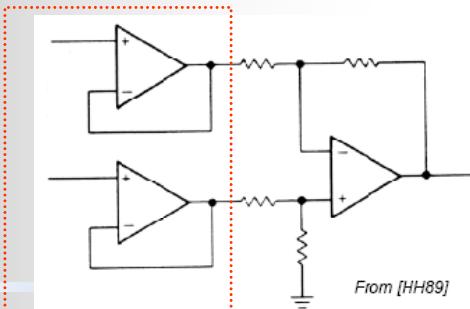
## Amplifier : Instrumentation Amplifier

- Terminologi INSTRUMENTATION AMPLIFIER digunakan untuk Differential Amplifier dengan
  - High Gain
  - Single ended Output
  - High input impedance
    - Dapat dilakukan dengan buffering
  - High CMRR



## Filter


- Filter digunakan untuk membuang sinyal dengan frekuensi yang tidak diinginkan
- Klasifikasi filter berdasarkan implementasi
  - Filter aktif** (termasuk rangkaian RC dan op-amp)
  - Filter pasif**
    - Terdiri atas rangkaian RLC
  - Filter digital**


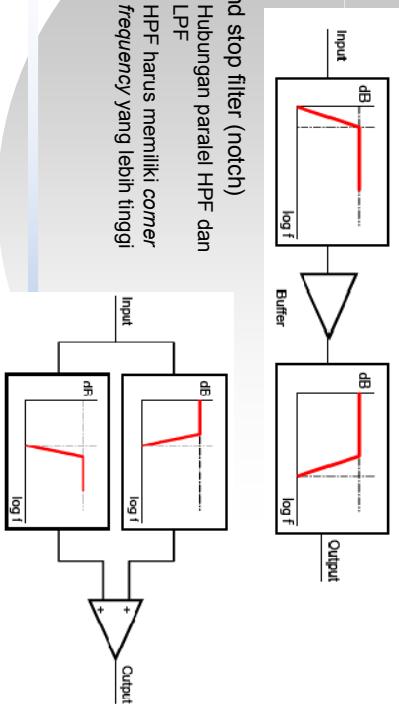
## SISTEM PENGUKURAN



- ❖ Bandpass filter
- Hubungan seri HPF & LPF
- HPF harus memiliki *corner frequency* yang lebih rendah
- Antar HPF dan LPF harus digunakan buffer



### Filter



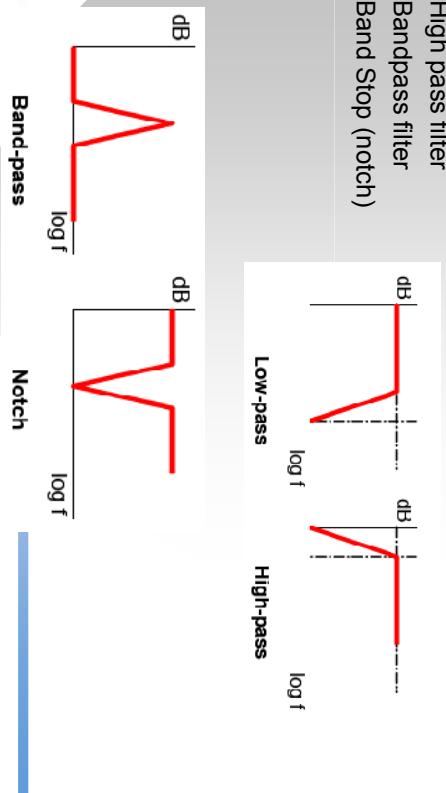
## SISTEM PENGUKURAN



Klasifikasi Filter berdasarkan respon frekuensi


- ❖ Low pass filter
- ❖ High pass filter
- ❖ Bandpass filter
- ❖ Band Stop (notch)




## SISTEM PENGUKURAN



❖ Low pass filter

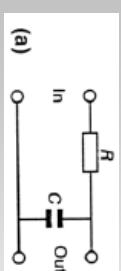


❖ High pass filter

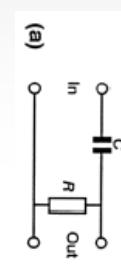
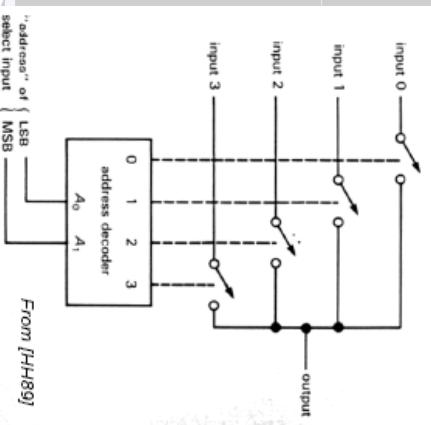
## SISTEM PENGUKURAN




- ❖ Rangkaian untuk memilih salah satu input dengan sinyal kontrol digital



### Multiplexer



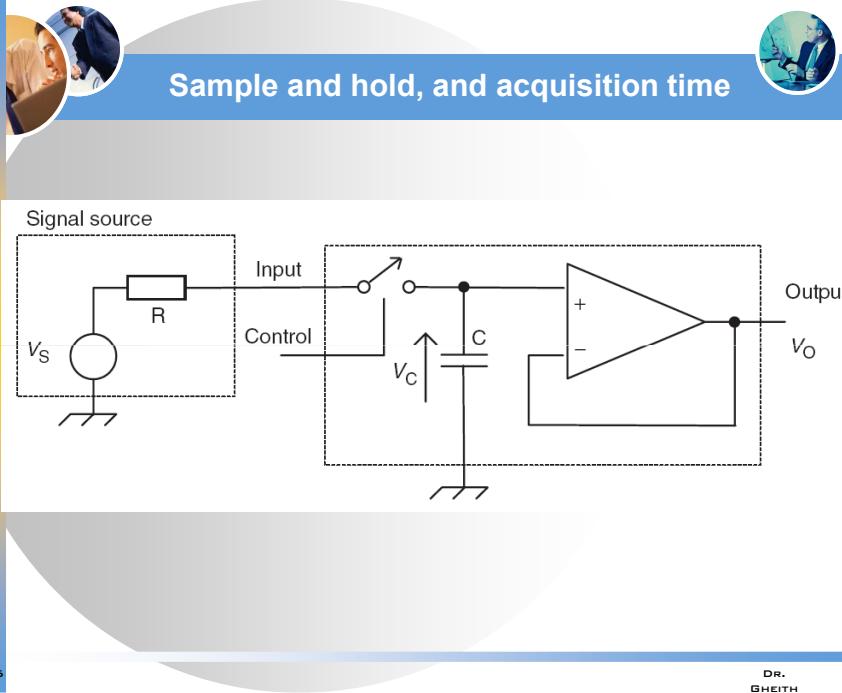


## Sample and hold, and acquisition time



## Analog to Digital Converter

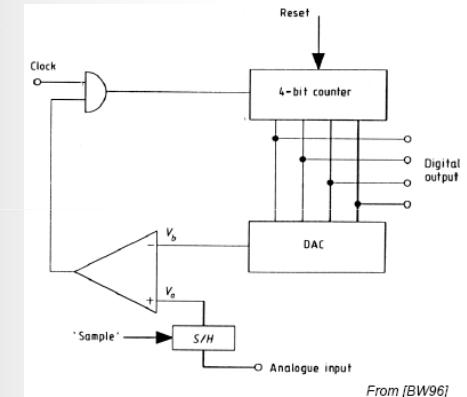
### Single Slope atau Ramp ADC

- ❖ Terdiri atas
  - Counter biner
  - DAC
  - Komparator analog
- ❖ Cara kerja
  - Reset counter
  - Input analog dicacah
  - Jika  $V_A > V_B$  counter naik
  - Jika  $V_A = V_B$  counter berhenti dan kode biner merupakan output
- ❖ Karakteristik
  - Relatif lambat karena waktu konversi dapat mencapai  $2^N$ , dimana N adalah resolusi ADC


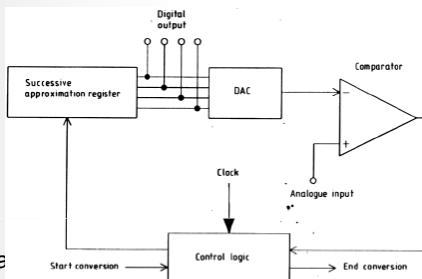
### Successive approximation ADC

- ❖ Terdiri atas
  - DAC
  - Komparator analog
  - Modul logic kontrol
  - Successive Approx Register
- ❖ Cara kerja
  - Kondisi awal : semua bit sama dengan NOL kemudian dimulai dengan MSB sama dengan 1 (10000.....0)
    - Jika analog input lebih besar, maka MSB = 1 atau MSB = 0
    - Register melakukan operasi yang sama dari MSB ke LSB




## Digital to Analog Converter

DR. GHEITH


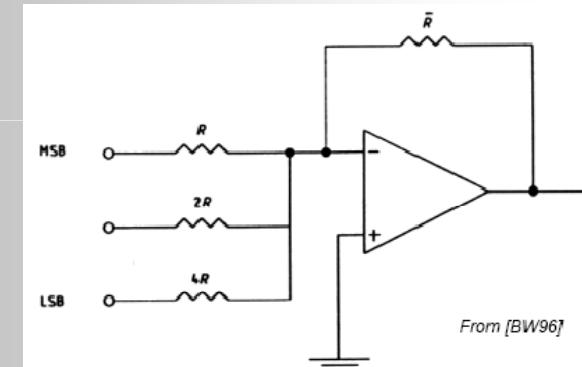
### Binary weighted ladder

- Setiap input diberi bobot oleh masing-masing resistor pada rangkaian op-amp



From [BW96]

## Data Acquisition System

- ❖ Introduction
- ❖ Components of DAS
- ❖ Methodology
- ❖ Types of Data Acquisition System
- ❖ Applications

29



## Introduction



- ❖ **Data acquisition systems**, as the name implies, are products or processes used to collect information to document or analyze some phenomenon.
- ❖ **Data acquisition** and data acquisition systems typically involves the conversion of analog waveforms into digital values for processing by computer.

30



## Methodology



### Source

Data acquisition begins with the physical phenomenon to be measured. Eg. of this include temperature, light intensity, gas pressure, fluid flow, and force. The values of these quantities must first be transformed into a unified form that can be sampled by a data acquisition system. The task of performing such transformations falls on devices called **sensors**.

### Signals

Signals may be digital (also called **logic signals** sometimes) or analog depending on the transducer used. Signal conditioning may be necessary if the signal from the transducer is not suitable for the DAQ hardware being used. The signal may need to be amplified, filtered or demodulated.

31

## Components of DAS


- ❖ The components of data acquisition systems include:
  - Sensors that convert physical parameters to electrical signals.
  - Signal conditioning circuitry to convert sensor signals into a form that can be converted to digital values.
  - Analog-to-digital converters, which convert conditioned sensor signals to digital values.



32




## Types of DAS

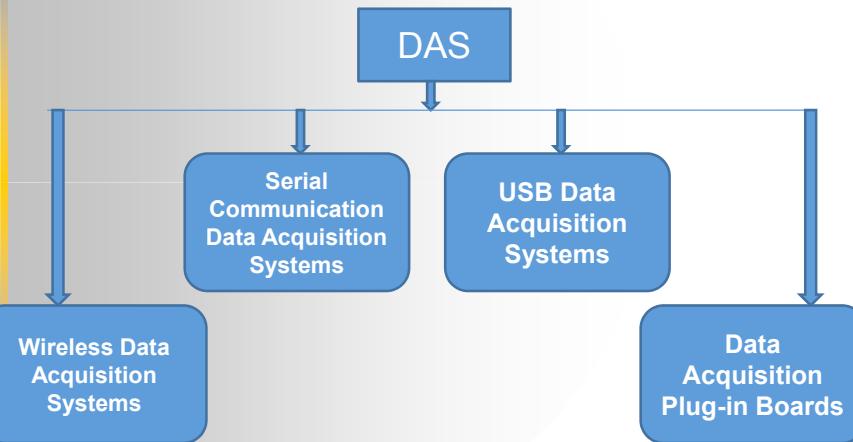

33

34

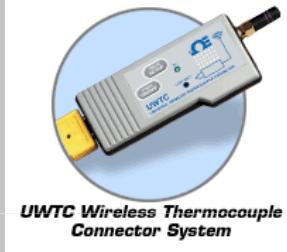

**UWTC Wireless Thermocouple Connector System**



**iDRX Series Serial Port**



**OMB-DAG-3000 Series USB Data Acquisition Modules**



**OME-PCI-1000 Series Data Acquisition Plug-in Boards**

## Applications

- Measure & Visualize
  - Quick measurements
  - Real-time data visualization
- Control
  - PC-based industrial automation
  - PID and other closed-loop control
- Test Automation
  - Design validation and verification
  - Manufacturing test automation
- Monitoring
  - Alarming and notification
  - Long-term data trending
- Prototyping
  - Functional prototypes
  - Customer proof of concepts

35

36

## Data Loggers

- Introduction
- Instrumentation Protocols
- Types
- Choosing a Data Logger
- Applications
- Data logging versus data acquisition**



## Introduction

- ❖ A **data logger** (also **data recorder**) is an electronic device that records data over time or in relation to location either with a built in or via external instruments and sensors
- ❖ Data loggers are available in various shapes and sizes.
- ❖ The range includes simple economical single channel fixed function loggers to more powerful programmable devices capable of handling hundreds of inputs.
- ❖ Simple single channel data loggers cost as little as \$25. More complicated loggers may costs hundreds or thousands of dollars

## Choosing a Data Logger

- ❖ Input Signal
- ❖ Number of Inputs
- ❖ Size
- ❖ Speed/Memory
- ❖ Real Time Operation

## Types of Data Loggers



**OM-CP-TEMP100**  
Single Input Logger



**OM-CP-QUADTEMP**  
Fixed Input Logger



**OM-DAQPRO-5300**  
Portable Datalogger



**OM-320**  
Modular Logger

## Examples

- ❖ A flight data recorder (FDR),
- ❖ An event data recorder (EDR),
- ❖ A voyage data recorder (VDR),
- ❖ Ultra Wideband Data Recorder,
- ❖ A Depth Recorder



## Applications



- Unattended weather station recording (such as wind speed / direction, temperature, relative humidity, solar radiation).
- Unattended hydrographic recording (such as water level, water depth, water flow, water pH, water conductivity).
- Unattended soil moisture level recording.
- Unattended gas pressure recording.
- Offshore buoys for recording a variety of environmental conditions.
- Road traffic counting.
- Environmental monitoring.
- Vehicle Testing
- Monitoring of relay status in railway signalling.



## Data logging versus data acquisition



### Data logging

- ❖ Data logger is a data acquisition system
- ❖ Typically have slower sample rates.
- ❖ Data loggers are implicitly stand-alone devices
- ❖ Data loggers used magnetic tape , punched paper tape ,directly viewable recorders Such as strip chart recorders

### Data acquisition

- ❖ Data acquisition system is not necessarily a data logger.
- ❖ Typically have fast sample rates.
- ❖ Data acquisition system must remain tethered to a computer to acquire data.
- ❖ Data acquisition used Static RAM, flash memory, EEPROM.