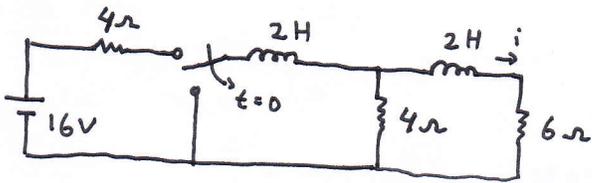



Find  $i$  for  $t > 0$  if the circuit is in steady state at  $t = 0^-$

9.3



Answer:

Circuit at  $t = 0^-$

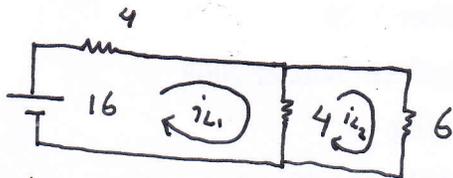

Loop  $i_{L1}$ :

$$-16 + 4i_{L1} + 4(i_{L1} - i_{L2}) = 0$$

$$8i_{L1} - 4i_{L2} = 16 \dots (1)$$

Loop  $i_{L2}$ :

$$4(i_{L2} - i_{L1}) + 6i_{L2} = 0$$

$$-4i_{L1} + 10i_{L2} = 0 \dots (2)$$

(1) & (2):

$$\begin{array}{r} 8i_{L1} - 4i_{L2} = 16 \quad \times 1 \\ -4i_{L1} + 10i_{L2} = 0 \quad \times 2 \\ \hline \end{array}$$


$$\begin{array}{r} 8i_{L1} - 4i_{L2} = 16 \\ -8i_{L1} + 20i_{L2} = 0 \\ \hline \end{array} +$$

$$16i_{L2} = 16$$

$$i_{L2} = 1$$

$$i_{L1} = \frac{10}{4} = 2,5$$

Circuit at  $t = 0^+$

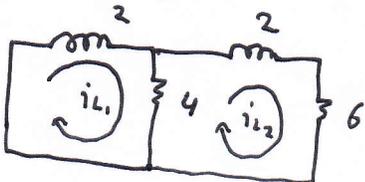

Loop  $i_{L1}$

$$2 \frac{di_{L1}}{dt} + 4(i_{L1} - i_{L2}) = 0$$

$$2 \frac{di_{L1}}{dt} + 4i_{L1} - 4i_{L2} = 0 \dots (3)$$

Loop  $i_{L2}$ :

$$4(i_{L2} - i_{L1}) + 2 \frac{di_{L2}}{dt} + 6i_{L2} = 0$$

$$4i_{L1} = 2 \frac{di_{L2}}{dt} + 10i_{L2} \dots (4)$$

differential:

$$4 \frac{di_{L1}}{dt} = 2 \frac{d^2 i_{L2}}{dt^2} + 10 \frac{di_{L2}}{dt} \times \frac{1}{2}$$

$$2 \frac{di_{L1}}{dt} = \frac{d^2 i_{L2}}{dt^2} + 5 \frac{di_{L2}}{dt} \dots (5)$$

(3), (4), (5):

$$\left( \frac{d^2 i_{L2}}{dt^2} + 5 \frac{di_{L2}}{dt} \right) + \left( 2 \frac{di_{L2}}{dt} + 10i_{L2} \right) - 4i_{L2} = 0$$

$$\frac{d^2 i_{L2}}{dt^2} + 7 \frac{di_{L2}}{dt} + 6i_{L2} = 0$$

Trans formasi:

$$s^2 + 7s + 6 = 0$$

$$(s+6)(s+1) = 0$$

$$s_1 = -1 \quad s_2 = -6$$

$$i_{L2} = A_1 \cdot e^{-t} + A_2 \cdot e^{-6t}$$

dari pers (v):

$$i_{L_1} = \frac{1}{2} \frac{di_{L_2}}{dt} + \frac{5}{2} i_{L_2}$$

$$= \frac{1}{2} (-A_1 e^{-t} - 6A_2 e^{-6t}) + \frac{5}{2} (A_1 e^{-t} + A_2 e^{-6t})$$

$$= 2A_1 e^{-t} - \frac{1}{2} A_2 e^{-6t}$$

Saat  $t=0$ :

$$\begin{array}{rcl} A_1 & + & A_2 & = & 1 \\ 2A_1 & - & \frac{1}{2}A_2 & = & \frac{5}{2} \end{array} \left. \vphantom{\begin{array}{rcl} A_1 & + & A_2 & = & 1 \\ 2A_1 & - & \frac{1}{2}A_2 & = & \frac{5}{2} \end{array}} \right\} \times 2$$

---

$$\begin{array}{rcl} A_1 & + & A_2 & = & 1 \\ 4A_1 & - & A_2 & = & 5 \end{array} +$$

$$5A_1 = 6$$

$$A_1 = \frac{6}{5} = 1,2$$

$$A_2 = 1 - A_1 = -0,2$$

$$\therefore i = i_{L_2} = 1,2 e^{-t} - 0,2 e^{-6t}$$