
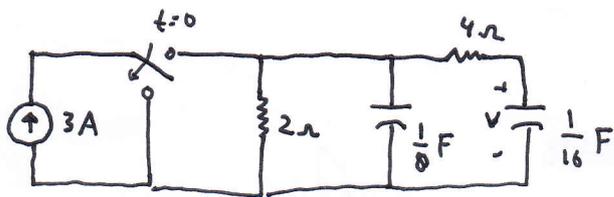


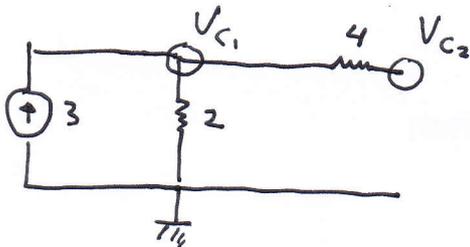Find  $v$  for  $t > 0$  if the circuit is in steady state at  $t = 0^-$  9.6




Answer:

Circuit at  $t = 0^-$



$$V_{c1} = V_{c2} = 3 \cdot 2 = 6 \text{ volt}$$

Circuit at  $t = 0^+$

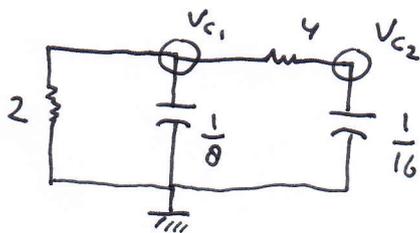

Node  $V_{c1}$ :

$$\frac{V_{c1}}{2} + \frac{1}{8} \frac{dV_{c1}}{dt} + \frac{V_{c1} - V_{c2}}{4} = 0 \quad \times 8$$

$$4V_{c1} + \frac{dV_{c1}}{dt} + 2V_{c1} - 2V_{c2} = 0$$

$$6V_{c1} + \frac{dV_{c1}}{dt} - 2V_{c2} = 0 \quad \dots (1)$$

Node  $V_{c2}$ :

$$\frac{V_{c2} - V_{c1}}{4} + \frac{1}{16} \frac{dV_{c2}}{dt} = 0 \quad \times 16$$

$$4V_{c2} - 4V_{c1} + \frac{dV_{c2}}{dt} = 0 \quad \dots (2)$$

$$4V_{c1} = \frac{dV_{c2}}{dt} + 4V_{c2}$$

$$V_{c1} = \frac{1}{4} \frac{dV_{c2}}{dt} + V_{c2} \quad \dots (3)$$

$$\frac{dV_{c1}}{dt} = \frac{1}{4} \frac{d^2V_{c2}}{dt^2} + \frac{dV_{c2}}{dt} \quad \dots (4)$$

(1), (3) & (4)

$$\left( \frac{6}{4} \frac{dV_{c2}}{dt} + 6V_{c2} \right) + \left( \frac{1}{4} \frac{d^2V_{c2}}{dt^2} + \frac{dV_{c2}}{dt} \right) -$$

$$2V_{c2} = 0$$

$$\frac{1}{4} \frac{d^2V_{c2}}{dt^2} + \frac{10}{4} \frac{dV_{c2}}{dt} + 4V_{c2} = 0 \quad \times 4$$

$$\frac{d^2V_{c2}}{dt^2} + 10 \frac{dV_{c2}}{dt} + 16V_{c2} = 0$$

transformasi:

$$s^2 + 10s + 16 = 0$$

$$(s+8)(s+2) = 0$$

$$V_{c2} = A_1 \cdot e^{-2t} + A_2 \cdot e^{-8t}$$

$$\begin{aligned} V_{c1} &= \frac{1}{4} (-2A_1 e^{-2t} - 8A_2 e^{-8t}) + \\ & A_1 e^{-2t} + A_2 e^{-8t} \\ &= \frac{1}{2} A_1 e^{-2t} - A_2 e^{-8t} \end{aligned}$$

Saat  $t = 0$ :

$$A_1 + A_2 = 6$$

$$\frac{1}{2} A_1 - A_2 = 6 \quad +$$

$$\frac{3}{2} A_1 = 12$$


$$A_1 = 12 \times \frac{2}{3} = 8$$

$$A_2 = 6 - A_1 = -2$$


$$\therefore \underline{v = 8e^{-2t} - 2e^{-8t}}$$

Using EWB for solving Problem 9.6

EWB

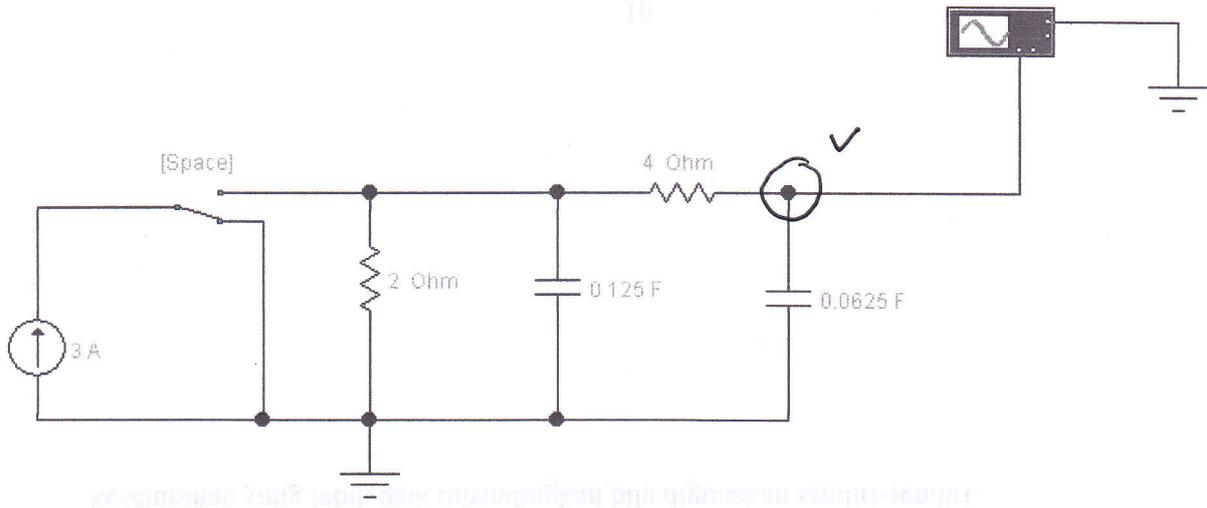


Example EWB Simulation

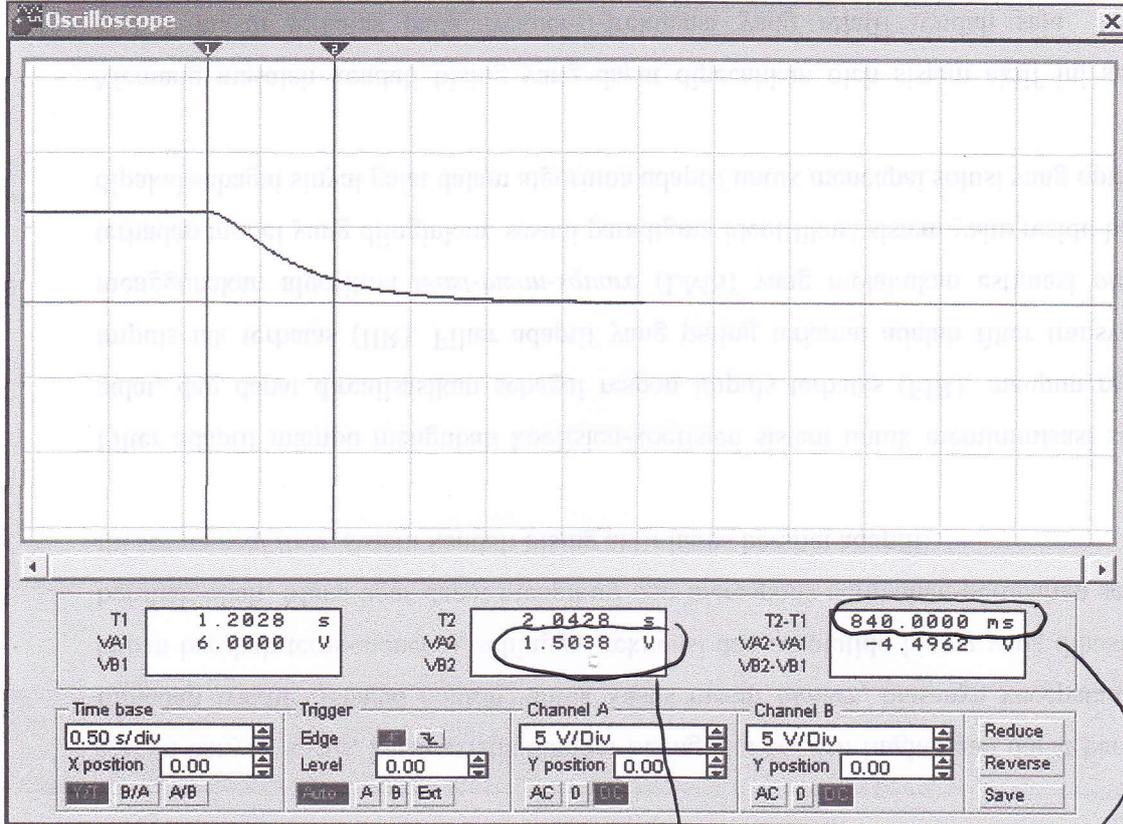

at  $t = 840 \text{ ms}$   
 $V = 1,5038 \text{ V}$

from analysis:
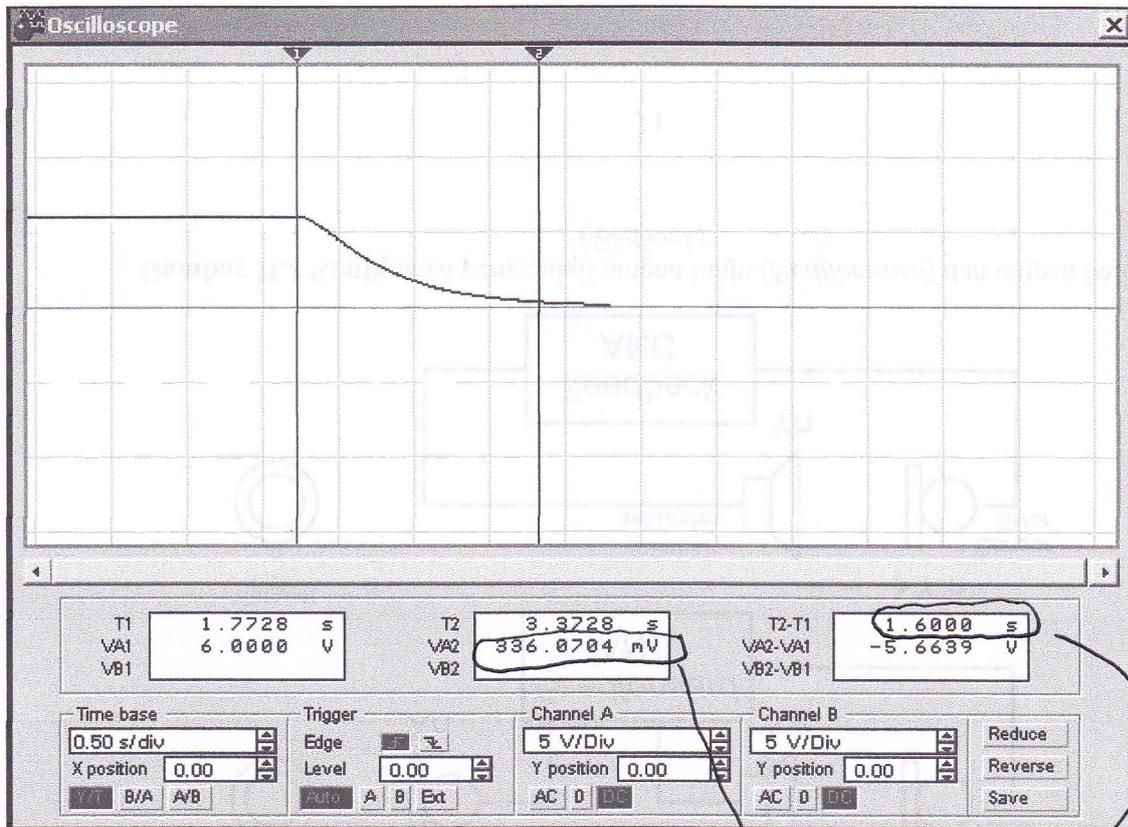
$$\begin{aligned}
 \text{at } t = 0,84 \text{ s, } V &= 8 \cdot e^{-2 \cdot 0,84} - 2 \cdot e^{-8 \cdot 0,84} \\
 &= 1,488579
 \end{aligned}$$



at  $t = 1,6 \text{ s}$   
 $V = 336,0704 \text{ mV}$

from analysis:

$$\text{at } t = 1,6 \text{ s, } V = 8 \cdot e^{-2 \cdot 1,6} - 2 \cdot e^{-8 \cdot 1,6}$$

$$= 0,326092 \text{ V}$$