
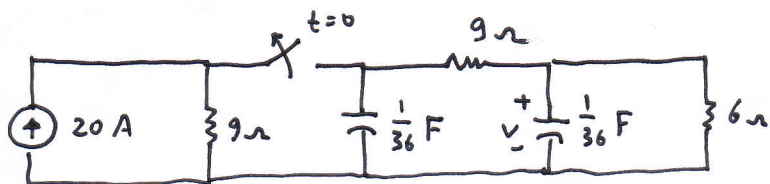


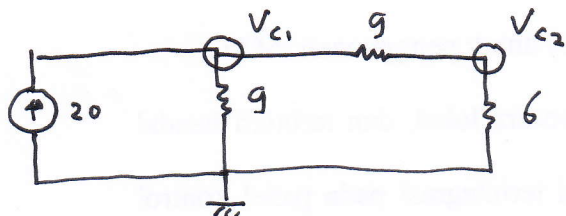9.9 Find  $v$  for  $t > 0$  if the circuit is in steady state at  $t = 0^-$



Answer

Circuit at  $t = 0^-$



Node  $V_{C1}$ :

$$-20 + \frac{V_{C1}}{9} + \frac{V_{C1} - V_{C2}}{9} = 0 \quad \times 9$$

$$2V_{C1} - V_{C2} = 180 \quad \dots (1)$$

Node  $V_{C2}$ :

$$\frac{V_{C2} - V_{C1}}{9} + \frac{V_{C2}}{6} = 0 \quad \times 54$$

$$6V_{C2} - 6V_{C1} + 9V_{C2} = 0$$

$$15V_{C2} - 6V_{C1} = 0 \quad \dots (2)$$

(1) & (2):

$$\begin{array}{r|l} 2V_{C1} - V_{C2} = 180 & \times 3 \\ -6V_{C1} + 15V_{C2} = 0 & \times 1 \end{array}$$

$$6V_{C1} - 3V_{C2} = 3 \cdot 180$$


$$-6V_{C1} + 15V_{C2} = 0$$

$$12V_{C2} = 3 \cdot 180$$

$$V_{C2} = 45$$

$$V_{C1} = \frac{180 + V_{C2}}{2} = 112,5$$

Circuit at  $t = 0^+$

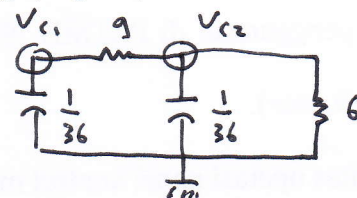

Node  $V_{C1}$ :

$$\frac{1}{36} \frac{dV_{C1}}{dt} + \frac{V_{C1} - V_{C2}}{9} = 0 \quad \times 36$$

$$\frac{dV_{C1}}{dt} + 4V_{C1} - 4V_{C2} = 0 \quad \dots (3)$$

Node  $V_{C2}$ :

$$\frac{V_{C2} - V_{C1}}{9} + \frac{1}{36} \frac{dV_{C2}}{dt} + \frac{V_{C2}}{6} = 0 \quad \times 36$$

$$4V_{C2} - 4V_{C1} + \frac{dV_{C2}}{dt} + V_{C2} = 0$$

$$4V_{C1} = \frac{dV_{C2}}{dt} + 5V_{C2} \quad \dots (4)$$

$$V_{C1} = \frac{1}{4} \frac{dV_{C2}}{dt} + \frac{5}{4} V_{C2}$$

$$\frac{dV_{C1}}{dt} = \frac{1}{4} \frac{d^2 V_{C2}}{dt^2} + \frac{5}{4} \frac{dV_{C2}}{dt} \quad \dots (5)$$

(3), (4), (5):

$$\left( \frac{1}{4} \frac{d^2 V_{C_2}}{dt^2} + \frac{10}{4} \frac{dV_{C_2}}{dt} \right) + \left( \frac{dV_{C_2}}{dt} + 10V_{C_2} \right) - 4V_{C_2} = 0$$

$$\frac{1}{4} \frac{d^2 V_{C_2}}{dt^2} + \frac{14}{4} \frac{dV_{C_2}}{dt} + 6V_{C_2} = 0 \quad \times 4$$

$$\frac{d^2 V_{C_2}}{dt^2} + 14 \frac{dV_{C_2}}{dt} + 24 V_{C_2} = 0$$

transformasi:

$$s^2 + 14s + 24 = 0$$

$$(s + 2)(s + 12) = 0$$

$$s_1 = -2 \quad s_2 = -12$$

$$V_{C_2} = A_1 e^{-2t} + A_2 e^{-12t} \quad (6)$$

$$V_{C_1} = \frac{1}{4} \frac{dV_{C_2}}{dt} + \frac{10}{4} V_{C_2}$$

$$= \frac{1}{4} (-2A_1 e^{-2t} - 12A_2 e^{-12t}) +$$

$$\frac{10}{4} (A_1 e^{-2t} + A_2 e^{-12t})$$

$$= 2A_1 e^{-2t} - \frac{1}{2} A_2 e^{-12t} \quad (7)$$

saat  $t=0$

$$\begin{array}{rcl} A_1 + A_2 = 45 & | & \times 1 \\ 2A_1 - \frac{1}{2} A_2 = 112,5 & | & \times 2 \end{array}$$

$$\begin{array}{rcl} A_1 + A_2 = 45 \\ 4A_1 - A_2 = 225 & + & \end{array}$$

$$A_1 = \frac{270}{5} = 54$$

$$A_2 = 45 - A_1 = -9$$

$$\therefore V = V_C = 54 e^{-2t} - 9 e^{-12t}$$