
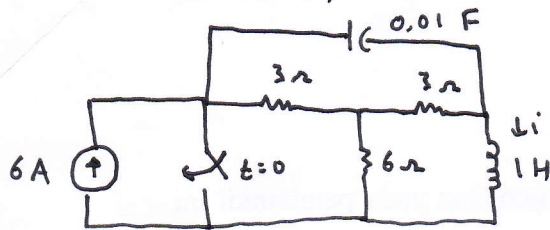


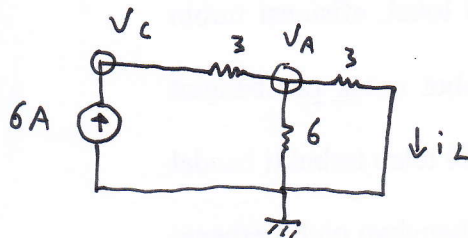9.11. Find  $i$  for  $t > 0$  if the circuit is in steady state at  $t = 0^-$



Answer

Circuit at  $t = 0^-$



Node  $V_c$ :

$$-6 + \frac{V_c - V_A}{3} = 0 \quad \times 3$$

$$V_c - V_A = 18$$

$$V_A = V_c - 18 \quad \dots (1)$$

node  $V_A$ :

$$\frac{V_A - V_c}{3} + \frac{V_A}{6} + \frac{V_A}{3} = 0 \quad \times 6$$

$$2V_A - 2V_c + V_A + 2V_A = 0$$

$$5V_A = 2V_c \quad \dots (2)$$

(1) & (2)

$$5(V_c - 18) = 2V_c$$


$$5V_c - 2V_c = 5 \cdot 18$$

$$V_c = \frac{5 \cdot 18}{3} = \underline{30}$$

$$V_A = 12$$

$$i_L = \frac{V_A}{3} = \underline{4A}$$

Circuit at  $t = 0^+$ :

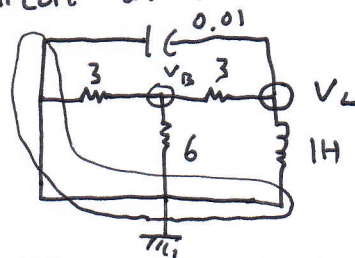

Node  $V_B$ :

$$\frac{V_B}{3} + \frac{V_B}{6} + \frac{V_B - V_L}{3} = 0 \quad \times 6$$

$$2V_B + V_B + 2V_B - 2V_L = 0$$

$$V_B = \frac{2}{5} V_L$$

Node  $V_L$ :

$$+ \frac{1}{100} \frac{\partial V_L}{\partial t} + \frac{V_L - V_B}{3} + \int V_L dt + k = 0$$

$$+ \frac{1}{100} \frac{\partial V_L}{\partial t} + \frac{3V_L}{15} + \int V_L dt + k = 0 \quad \times 100$$

$$+ \frac{\partial V_L}{\partial t} + 20V_L + 100 \int V_L dt + k = 0$$

differential:

$$\frac{\partial^2 V_L}{\partial t^2} + 20 \frac{\partial V_L}{\partial t} + 100 V_L = 0$$

transformasi:

$$s^2 + 20s + 100 = 0$$

$$(s + 10)(s + 10) = 0$$

$$V_L = (A_1 + A_2 t) \cdot e^{-10t}$$

$$V_L = (A_1 + A_2 t) \cdot e^{-10t}$$

$$i_L = \frac{1}{L} \int V_L dt + i_0$$

$$i_L \approx (C_1 + C_2 t) e^{-10t}$$

$$V_L = C_2 e^{-10t} + (C_1 + C_2 t) \cdot -10 e^{-10t}$$

$$= -V_c$$

at  $t = 0$ :

$$4 = (C_1 + C_2 t) e^{-10t}$$

$$C_1 = 4$$

$$-30 = C_2 + -10C_1$$

$$C_2 = -30 + 10 \cdot 4 = 10$$

$$\therefore i = (4 + 10t) e^{-10t}$$

Tabel 7-2 Perbandingan MSE dan SER simulasi identifikasi

Algoritma	MSE	SER
Fast LMS	$7.8 \times 10^{-4}$	14.39%
Fast LMS II	$6 \times 10^{-4}$	14.73 dB
RLS	$7.3 \times 10^{-4}$	9.106 dB