
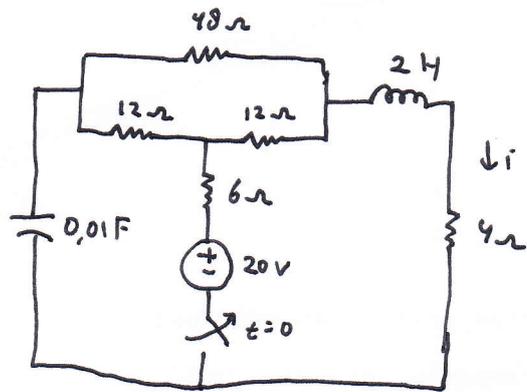


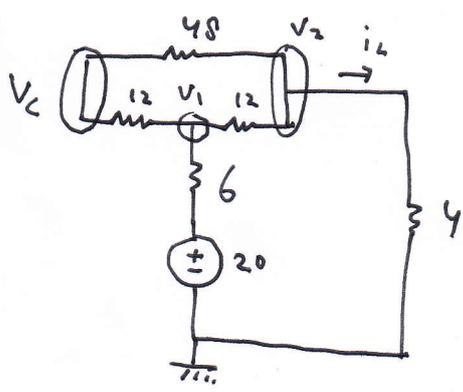9.13 Find  $i$  for  $t > 0$  if the circuit is in steady state at  $t = 0^-$



Circuit at  $t = 0^-$



node  $V_c$ :

$$\frac{V_c - V_1}{12} + \frac{V_c - V_2}{48} = 0 \quad \times 48$$

$$4V_c - 4V_1 + V_c - V_2 = 0$$

$$5V_c - 4V_1 - V_2 = 0 \quad \dots (1)$$

node  $V_1$ :

$$\frac{V_1 - V_c}{12} + \frac{V_1 - V_2}{12} + \frac{V_1 - 20}{6} = 0 \quad \times 12$$

$$V_1 - V_c + V_1 - V_2 + 2V_1 - 40 = 0$$

$$4V_1 - V_c - V_2 = 40 \quad \dots (2)$$

node  $V_2$ :

$$\frac{V_2 - V_c}{48} + \frac{V_2 - V_1}{12} + \frac{V_2}{4} = 0 \quad \times 48$$

$$V_2 - V_c + 4V_2 - 4V_1 + 12V_2 = 0$$

$$17V_2 - 4V_1 - V_c = 0 \quad \dots (3)$$

(1) & (2):

$$\begin{array}{r} -4V_1 + 5V_c - V_2 = 0 \\ 4V_1 - V_c - V_2 = 40 \\ \hline 4V_c - 2V_2 = 40 \quad \dots (4) \end{array}$$

(2) & (3):

$$\begin{array}{r} 4V_1 - V_c - V_2 = 40 \\ -4V_1 - V_c + 17V_2 = 0 \\ \hline -2V_c + 16V_2 = 40 \quad \dots (5) \end{array}$$


(4) & (5):

$$\begin{array}{r} 4V_c - 2V_2 = 40 \quad | \times 8 \\ -2V_c + 16V_2 = 40 \quad | \times 1 \\ \hline 30V_c - 16V_2 = 320 \\ -2V_c + 16V_2 = 40 \quad + \\ \hline 30V_c = 360 \\ V_c = 12 \end{array}$$

$$V_2 = \frac{4V_c - 40}{2} = 4$$

$$i_L = \frac{V_2}{4} = 1 \text{ A}$$


Circuit at  $t = 0^+$

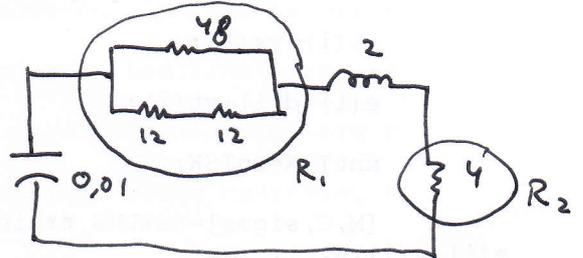

$$R_1 = \frac{(12+12) \times 48}{(12+12)+48} = \frac{24 \times 48}{72} = 16$$

$$R_1 + R_2 = 20$$

Equivalent circuit:

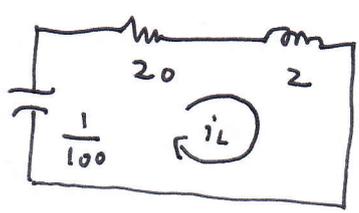

loop  $i_L$ :

$$\frac{1}{0,01} \int i_L dt + K + 20 i_L + 2 \frac{di_L}{dt} = 0$$

diff.

$$100 i_L + 20 \frac{di_L}{dt} + 2 \frac{di_L}{dt} = 0 \quad \times \frac{1}{2}$$

$$\frac{di_L}{dt^2} + 10 \frac{di_L}{dt} + 50 i_L = 0$$

transformasi:

$$s^2 + 10s + 50 = 0$$

$$s_{1,2} = \frac{-10 \pm \sqrt{100 - 200}}{2} = -5 \pm 5j$$

$$i_L = e^{-5t} (B_1 \sin(5t) + B_2 \cos(5t))$$

$$V_L = L \frac{di_L}{dt}$$

$$= 2 \left( -5 e^{-5t} (B_1 \sin 5t + B_2 \cos 5t) + e^{-5t} (5B_1 \cos 5t - 5B_2 \sin 5t) \right)$$

$$= 2 \left( -5B_1 e^{-5t} \sin 5t - 5B_2 e^{-5t} \cos 5t + 5B_1 e^{-5t} \cos 5t - 5B_2 e^{-5t} \sin 5t \right)$$

$$= (-10B_1 - 10B_2) e^{-5t} \sin 5t + (-10B_2 + 10B_1) e^{-5t} \cos 5t$$

$$= -10(B_1 + B_2) e^{-5t} \sin 5t + 10(B_1 - B_2) e^{-5t} \cos 5t$$

$$V_C = -V_R - V_L$$

$$= -20(B_1 e^{-5t} \sin 5t + B_2 e^{-5t} \cos 5t) + 10(B_1 + B_2) e^{-5t} \sin 5t - 10(B_1 - B_2) e^{-5t} \cos 5t$$

at  $t=0$ :

$$i_L = 1 = B_2$$

$$V_C = 12 = -20B_2 - 10(B_1 - B_2)$$

$$12 = -20B_2 + 10B_2 - 10B_1$$

$$12 = -10B_2 - 10B_1$$

$$B_1 = \frac{12 - 10}{10} = 0,2$$

$$\therefore i = e^{-5t} (0,2 \sin 5t + \cos 5t)$$