
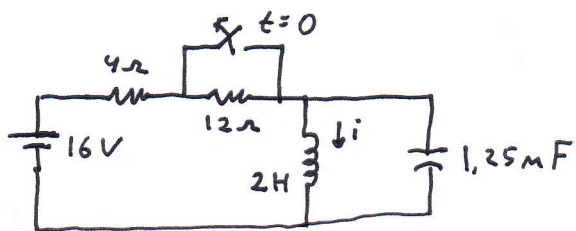


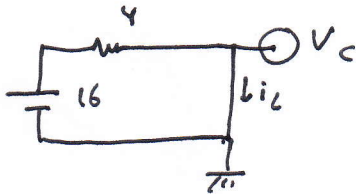9.17

Find i for $t > 0$ if the circuit is in steady state at $t = 0^-$




Circuit at $t = 0^-$



$$i_L = \frac{16}{4} = 4A$$

$$V_C = 0$$

Circuit at $t = 0^+$

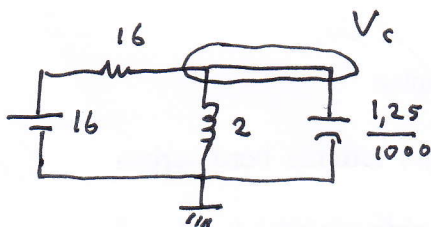

node V_C :

$$\frac{V_C - 16}{16} + \frac{1}{2} \int V_C dt + k + \frac{1.25}{1000} \frac{dV_C}{dt} = 0$$

$$\frac{V_C - 16}{16} + \frac{1}{2} \int V_C dt + k + \frac{1}{800} \frac{dV_C}{dt} = 0 \quad \times 800$$

$$50V_C - 50 \cdot 16 + 400 \int V_C dt + k + \frac{dV_C}{dt} = 0$$

diff:

$$50 \frac{dV_C}{dt} + 400 V_C + \frac{d^2 V_C}{dt^2} = 0$$

Transformasi:

$$s^2 + 50s + 400 = 0$$

$$s_{1,2} = \frac{-50 \pm \sqrt{2500 - 1600}}{2} = \frac{-50 \pm \sqrt{900}}{2}$$

$$= -25 \pm 15$$

$$s_1 = -40 \quad s_2 = -10$$

$$V_{CN} = A_1 e^{-40t} + A_2 e^{-10t}$$

$$i_{LN} = \frac{1}{L} \int V_{CN} dt$$

$$\approx C_1 e^{-40t} + C_2 e^{-10t}$$


$$V_{LN} = L \frac{di_{LN}}{dt}$$

$$= 2 \cdot 40 C_1 e^{-40t} - 2 \cdot 10 C_2 e^{-10t}$$

$$= -80 C_1 e^{-40t} - 20 C_2 e^{-10t}$$

force response untuk constant forcing dapat diperoleh dari keadaan steady state.

Circuit at steady state:

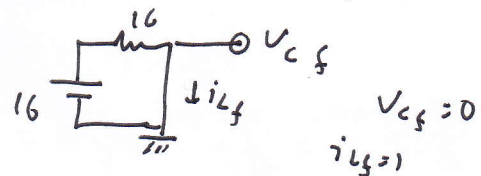

complete response:

$$i_L = i_{LN} + i_{Lf}$$

$$V_C = V_{CN} + V_{Cf}$$

at $t = 0$

$$i_L = 4 = C_1 + C_2 + 1$$

$$V_C = 0 = -80 C_1 - 20 C_2$$

$$C_1 + C_2 = 3 \quad \times 20$$

$$-80 C_1 - 20 C_2 = 0 \quad \times 1$$

$$20 C_1 + 20 C_2 = 60$$

$$-80 C_1 - 20 C_2 = 0$$

$$-60 C_1 = 60$$

$$C_1 = -1$$

$$C_2 = 3 - C_1 = 4$$

$$\therefore i_L = -e^{-40t} + 4e^{-10t} + 1$$