
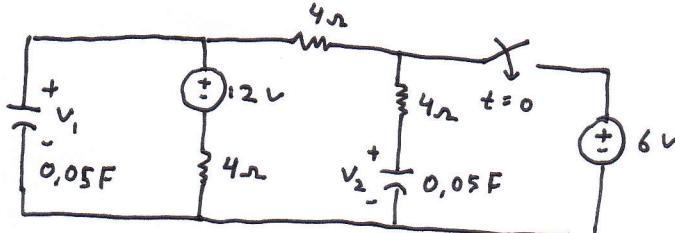


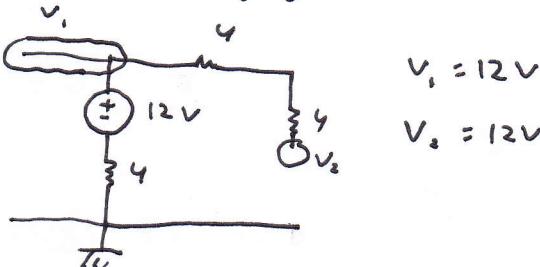9.21


Find v_1 and v_2 for $t > 0$ if the circuit is in steady state at $t = 0^-$.



Circuit at $t = 0^-$



Circuit at $t = 0^+$

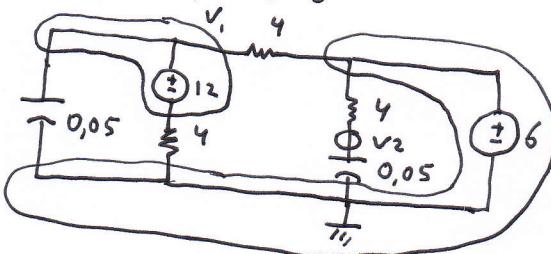

Node V_1 :

$$0,05 \frac{dV_1}{dt} + \frac{V_1 - 12}{4} + \frac{V_1 - 6}{4} = 0 \quad \times 4$$

$$0,2 \frac{dV_1}{dt} + V_1 - 12 + V_1 - 6 = 0$$

$$0,2 \frac{dV_1}{dt} + 2V_1 - 18 = 0 \quad \times 5$$

$$\frac{dV_1}{dt} + 10V_1 - 90 = 0$$

$$\frac{dV_1}{dt} + 10V_1 = 90$$

General equation

$$\frac{dy}{dt} + P_y = Q$$

$$y = e^{-P_t} \int Q e^{P_t} dt + A e^{-P_t}$$

$$V_1 = e^{-10t} \int_{90} e^{10t} dt + A e^{-10t}$$

$$V_1 = A \cdot e^{-10t} + \frac{90}{10} \cdot e^{-10t} \cdot e^{10t}$$

$$= A \cdot e^{-10t} + 9$$

at $t = 0$:

$$V_1 = 12 = A \cdot e^{-10t} + 9$$

$$A = 12 - 9 = 3$$

$$\therefore V_1 = 3e^{-10t} + 9$$

node V_2 :

$$\frac{V_2 - 6}{4} + 0,05 \frac{dV_2}{dt} = 0 \quad \times 20$$

$$5V_2 - 30 + \frac{dV_2}{dt} = 0$$

$$\frac{dV_2}{dt} + 5V_2 = 30$$

$$V_2 = e^{-5t} \int 30 e^{5t} dt + A e^{-5t}$$

$$= A \cdot e^{-5t} + 6$$

at $t = 0$

$$V_2 = 12 = A \cdot e^{-5t} + 6$$

$$A = 6$$

$$\therefore V_2 = 6 \cdot e^{-5t} + 6$$