
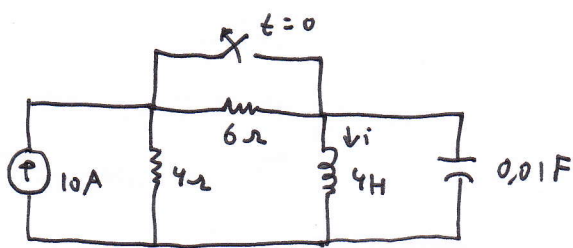


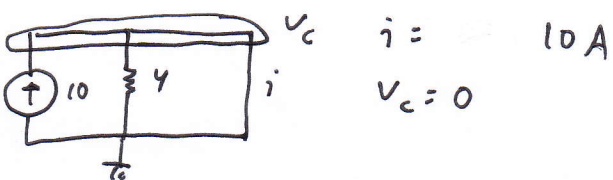
9.25 Find i for $t > 0$ if the circuit is in steady state at $t = 0^-$



circuit at $t = 0^-$



Circuit at $t = 0^+$

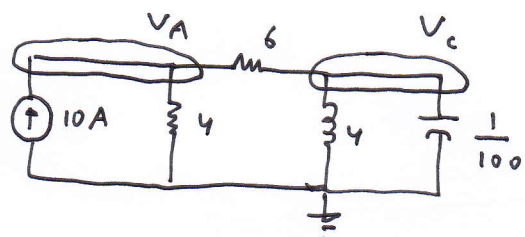

Node V_A :

$$-10 + \frac{V_A}{4} + \frac{V_A - V_C}{6} = 0 \quad \times 12$$

$$3V_A + 2V_A - 2V_C = 120$$

$$V_A = \frac{120 + 2V_C}{5}$$

Node V_C :

$$\frac{V_C - V_A}{6} + \frac{1}{4} \int V_C dt + k + \frac{1}{100} \frac{dV_C}{dt} = 0 \quad \times 300$$

$$50V_C - 50V_A + 75 \int V_C dt + k + 3 \frac{dV_C}{dt} = 0$$

$$50V_C - 50 \left(\frac{120 + 2V_C}{5} \right) + 75 \int V_C dt + k + 3 \frac{dV_C}{dt} = 0$$

$$50V_C - 1200 - 20V_C + 75 \int V_C dt + k + 3 \frac{dV_C}{dt} = 0$$

diff:

$$3 \frac{d^2 V_C}{dt^2} + 30 \frac{dV_C}{dt} + 75 V_C = 0 \quad \times \frac{1}{3}$$

$$\frac{d^2 V_C}{dt^2} - 10 \frac{dV_C}{dt} + 25 V_C = 0$$

transf:

$$s^2 + 10s + 25 = 0$$

$$(s+5)(s+5) = 0$$

$$s_1 = s_2 = -5$$


$$V_{CN} = (A_1 + A_2 t) \cdot e^{-5t}$$

$$i_{LN} = \frac{1}{L} \int V_{CN} dt \approx (C_1 + C_2 t) \cdot e^{-5t}$$

$$V_{LN} = L \frac{di_{LN}}{dt}$$

$$= 4(C_2 \cdot e^{-5t} - 5(C_1 + C_2 t) e^{-5t}) = 4C_2 e^{-5t} - 20C_1 e^{-5t} - 20C_2 t e^{-5t} = (4C_2 - 20C_1 - 20C_2 t) e^{-5t}$$

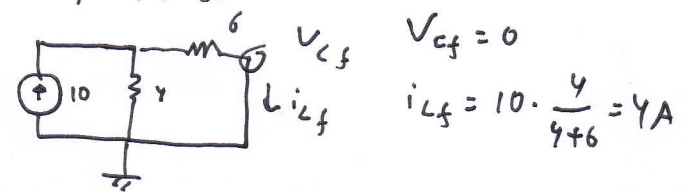forced response untuk constant forcing dapat diperoleh dari keadaan steady state:



complete response:

$$i_L = i_{LN} + i_{Lf} = (C_1 + C_2 t) e^{-5t} + 4$$

$$V_L = V_{LN} + V_{Lf} = (4C_2 - 20C_1 - 20C_2 t) e^{-5t}$$

at $t = 0$:

$$i = 10 = C_1 + 4 \Rightarrow C_1 = 6$$

$$V_C = V_L = 0 = 4C_2 - 20 \cdot 6$$

$$C_2 = \frac{20 \cdot 6}{4} = 30$$

$$\therefore i = (6 + 30t) e^{-5t} + 4$$