
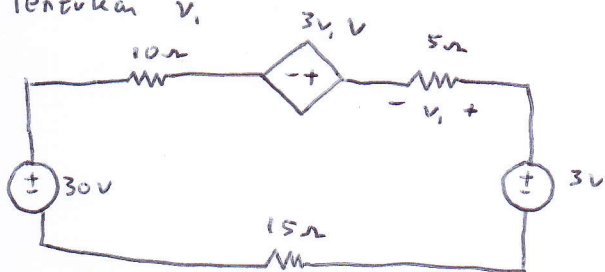


1. Tentukan V_1 .

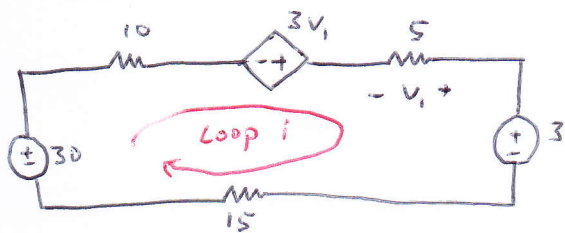

Jawab:



KVL loop i_1 :

$$-30 + 10i_1 - 3V_1 + 5i_1 + 3 + 15i_1 = 0$$

$$30i_1 - 3V_1 = 27 \quad \dots (1)$$

Dari resistor 5Ω :

$$5i_1 = -V_1$$

$$i_1 = -\frac{1}{5}V_1 \quad \dots (2)$$


(1) & (2):

$$30\left(-\frac{1}{5}V_1\right) - 3V_1 = 27$$


$$-6V_1 - 3V_1 = 27$$

$$V_1 = \frac{27}{-9} = \underline{\underline{-3 \text{ volt}}}$$

2. Tentukan V_1 dan i_1 .

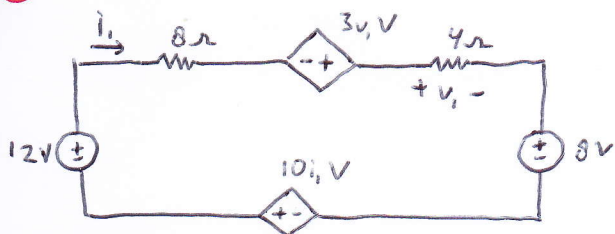

Jawab:

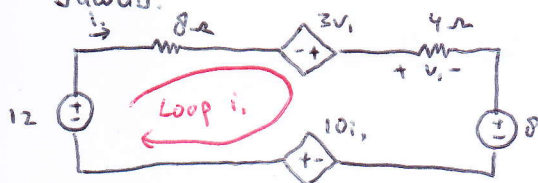

KVL loop i_1 :

$$-12 + 8i_1 - 3V_1 + 4i_1 + 8 - 10i_1 = 0$$

$$2i_1 - 3V_1 - 4 = 0 \quad \dots (1)$$

Dari resistor 4Ω :

$$4i_1 = V_1 \quad \dots (2)$$

(1) & (2):


$$2i_1 - 3(4i_1) - 4 = 0$$

$$2i_1 - 12i_1 = 4$$


$$i_1 = \frac{4}{-10} = -0,4 \text{ A}$$

$$V_1 = 4i_1 = -1,6 \text{ volt}$$

3. Tentukan i_1 .

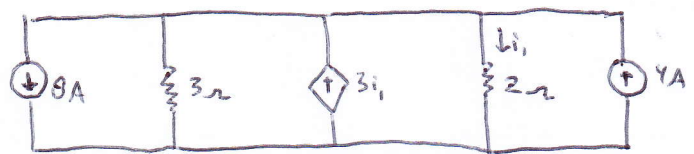

Jawab:

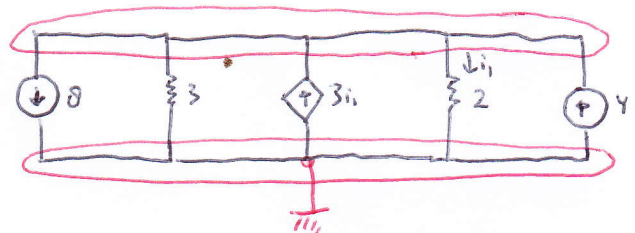

KCL node V :

$$8 + \frac{V}{3} - 3i_1 + \frac{V}{2} - 4 = 0 \quad \times 6$$

$$24 + 5V - 18i_1 = 0 \quad \dots (1)$$

Dari resistor 2Ω :

$$\frac{V}{2} = i_1$$

$$V = 2i_1 \quad \dots (2)$$

(1) & (2):

$$24 + 5(2i_1) - 18i_1 = 0$$


$$-8i_1 = -24$$

$$\underline{\underline{i_1 = 3 \text{ A}}}$$

4. Tentukan i jika:


(a) $R = 6\Omega$

(b) $R = 4,5\Omega$

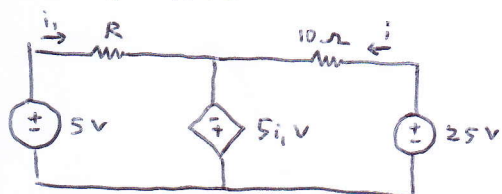

Jawab:

(a) Jika $R = 6\Omega$

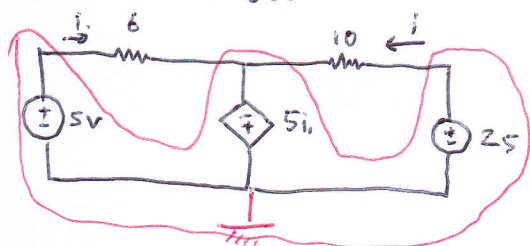


$$i_1 = \frac{5 - (-5i_1)}{6} = \frac{5 + 5i_1}{6}$$

$$6i_1 = 5 + 5i_1$$

$$i_1 = 5$$

$$i = \frac{25 - (-5i_1)}{10} = \frac{25 + 5(5)}{10} = 5 \text{ A}$$

(b) Jika $R = 4,5\Omega$

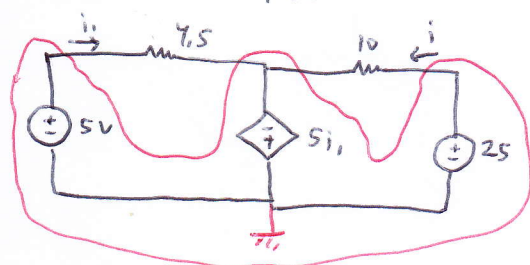

$$i_1 = \frac{5 - (-5i_1)}{4,5}$$


$$4,5i_1 = 5 + 5i_1$$

$$-0,5i_1 = 5$$


$$i_1 = \frac{5}{-0,5} = -10 \text{ A}$$

$$i = \frac{25 - (-5i_1)}{10} = \frac{25 + 5(-10)}{10} = -2,5 \text{ A}$$

5. Tentukan i_1 dan V

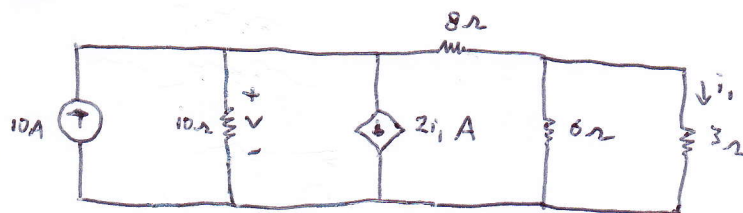

Jawab:

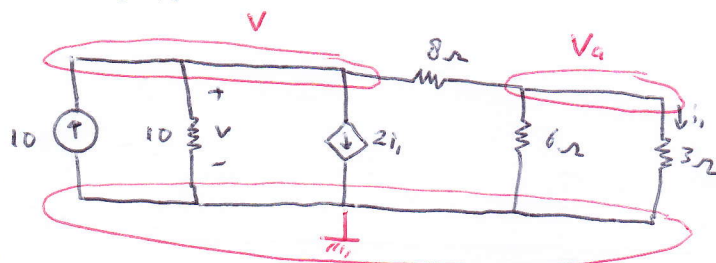

KCL node V :

$$-10 + \frac{V}{10} + 2i_1 + \frac{V - V_a}{8} = 0 \quad \times 40$$

$$-400 + 4V + 80i_1 + 5V - 5V_a = 0$$

$$-400 + 9V + 80i_1 - 5V_a = 0 \quad \dots (1)$$

KCL node V_a :

$$\frac{V_a - V}{8} + \frac{V_a}{6} + \frac{V_a}{3} = 0 \quad \times 24$$

$$3V_a - 3V + 4V_a + 8V_a = 0$$

$$15V_a = 3V$$

$$5V_a = V \quad \dots (2)$$

Resistor 3Ω :

$$i_1 = \frac{V_a}{3} \quad \dots (3)$$

$$(2) \& (3): i_1 = \frac{V}{15} \quad \dots (4)$$

(1), (2) & (4):

$$-400 + 9V + 80\left(\frac{V}{15}\right) - 5V = 0$$

$$8V + \frac{16V}{3} = 400 \quad \times 3$$


$$24V + 16V = 1200$$

$$V = \frac{1200}{40} = 30 \text{ volt}$$


dari (4):

$$i_1 = \frac{V}{15} = \frac{30}{15} = 2 \text{ A}$$

6. Tentukan i .

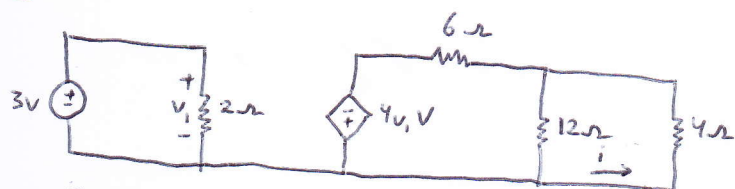

Jawab:

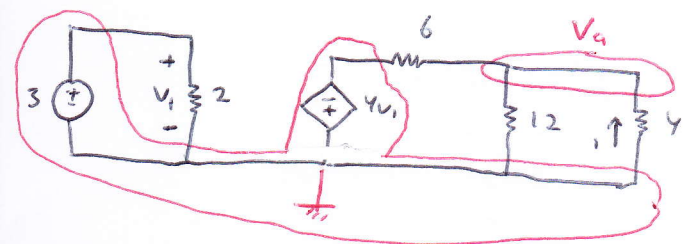

$$V_1 = 3 \text{ volt}$$

KCL node V_a :

$$\frac{V_a - (-4V_1)}{6} + \frac{V_a}{12} + \frac{V_a}{4} = 0 \quad \times 12$$


$$2V_a + 8V_1 + V_a + 3V_a = 0$$

$$6V_a + 8 \cdot 3 = 0$$


$$V_a = \frac{-24}{6} = -4 \text{ volt}$$

$$i = \frac{0 - V_a}{4} = \frac{0 - (-4)}{4} = 1 \text{ Ampere}$$

7. Tentukan V .

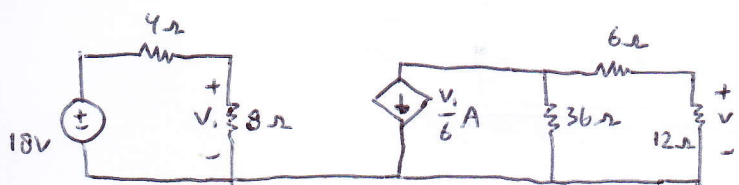

Jawab:

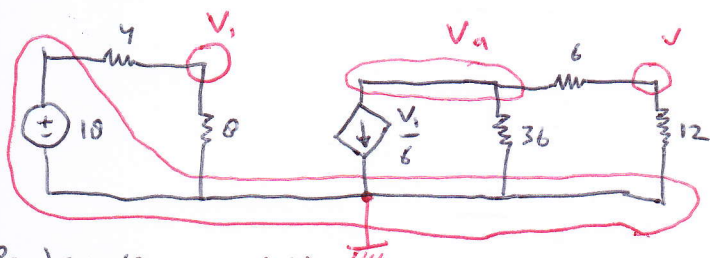

Pembagi tegangan di V_1 :

$$V_1 = \frac{8}{4+8} \cdot 18 = \frac{8}{12} \cdot 18 = 12 \text{ volt} \quad \dots (1)$$

KCL node V :

$$\frac{V}{12} + \frac{V - V_a}{6} = 0 \quad \times 12$$

$$V + 2V - 2V_a = 0$$

$$3V = 2V_a$$

$$V_a = \frac{3}{2} V \quad \dots (2)$$

KCL node V_a :

$$\frac{V_1}{6} + \frac{V_a}{36} + \frac{V_a - V}{6} = 0 \quad \times 36$$

$$6V_1 + V_a + 6V_a - 6V = 0$$

$$6V_1 + 7V_a - 6V = 0 \quad \dots (3)$$

(1) & (3):

$$6 \cdot 12 + 7V_a - 6V = 0 \quad \dots (4)$$

(4) & (2):


$$6 \cdot 12 + 7 \cdot \frac{3}{2} V - 6V = 0 \quad \times 2$$

$$12 \cdot 12 + 21V - 12V = 0$$


$$9V = -144$$

$$V = \frac{-144}{9} = -16 \text{ volt}$$

8. Tentukan i .

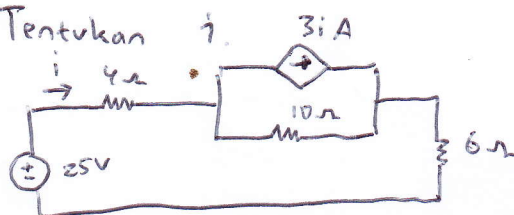

Jawab:

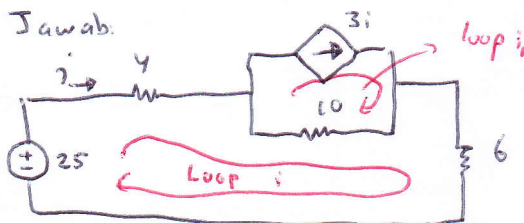

$$\text{Loop } i_1: i_1 = 3i \quad \dots (1)$$

loop i :

$$-25 + 4i + 10(i - i_1) + 6i = 0$$


$$-25 + 20i - 10i_1 = 0 \quad \dots (2)$$

(1) & (2):


$$20i - 10(3i) = 25$$

$$i = \frac{25}{-10} = -2,5 \text{ A}$$

9. Tentukan v

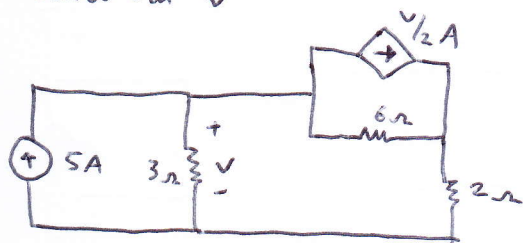

Jawab:

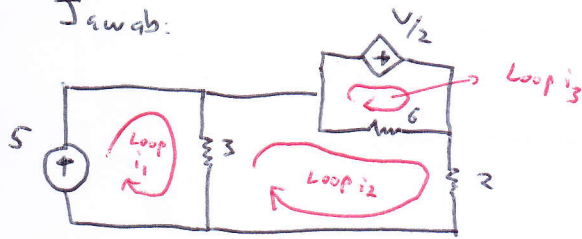

$$\text{Loop } i_1: \quad i_1 = 5A \quad \dots (1)$$

$$\text{Loop } i_3: \quad i_3 = \frac{V}{2} \quad \dots (2)$$

Loop i_2 :

$$3(i_2 - i_1) + 6(i_2 - i_3) + 2i_2 = 0$$

$$11i_2 - 3i_1 - 6i_3 = 0 \quad \dots (3)$$

dari resistor 3Ω :

$$\begin{aligned} V &= 3(i_1 - i_2) = 3i_1 - 3i_2 \\ &= 15 - 3i_2 \quad \dots (4) \end{aligned}$$

(1), (2), (3) & (4):

$$11i_2 - 3(5) - 6\left(\frac{V}{2}\right) = 0$$

$$11i_2 - 15 - 3(15 - 3i_2) = 0$$

$$11i_2 - 15 - 45 + 9i_2 = 0$$

$$20i_2 = 60$$

$$\text{dari (4):} \quad i_2 = 3$$

$$V = 15 - 3i_2$$

$$= 15 - 9 = \underline{\underline{6 \text{ volt}}}$$